

Chap. 3

Arithmetic for Computers


- 3.1 Introduction** 178
- 3.2 Addition and Subtraction** 178
- 3.3 Multiplication** 183
- 3.4 Division** 189
- 3.5 Floating Point** 196
- 3.6 Parallelism and Computer Arithmetic:**
Subword Parallelism 222
- 3.7 Real Stuff: Streaming SIMD Extensions and
Advanced Vector Extensions in x86** 224

Arithmetic for Computers

- Operations on **integers**
 - Addition and subtraction
 - Multiplication and division
 - Dealing with overflow
- Floating-point (浮動小數點) **real numbers**
 - Representation and operations

Integer Addition


- Example : 7 + 6

 


- Half Adder
- Full Adder
- Parallel Adder
- Carry Lookahead Adder

Integer Addition

- Example : 7 + 6

 

carry lookahead adder(CLA)

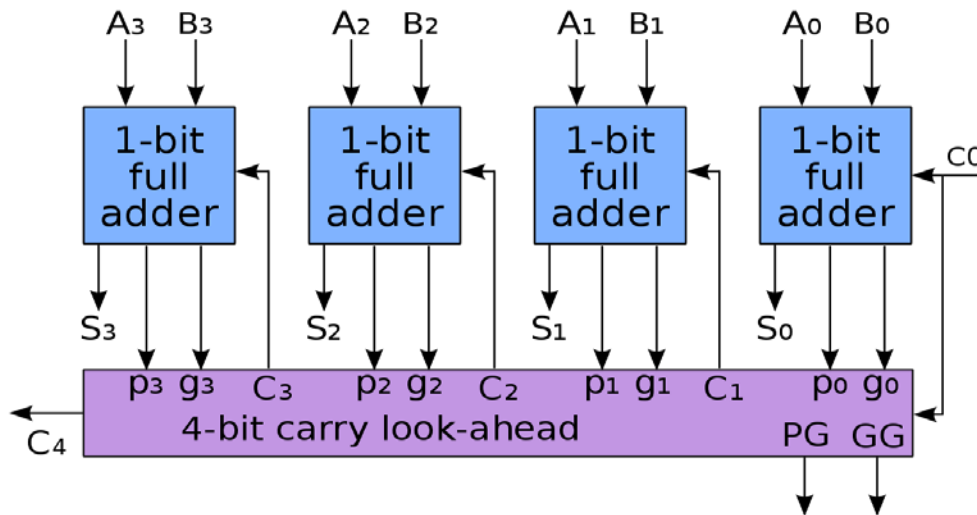


Integer Subtraction

- Add negation of second operand
- Example : $7 - 6 = 7 + (-6)$

+7: 0000 0000 ... 0000 0111
-6: 1111 1111 ... 1111 1010
+1: 0000 0000 ... 0000 0001


- Binary Adder/Subtractor

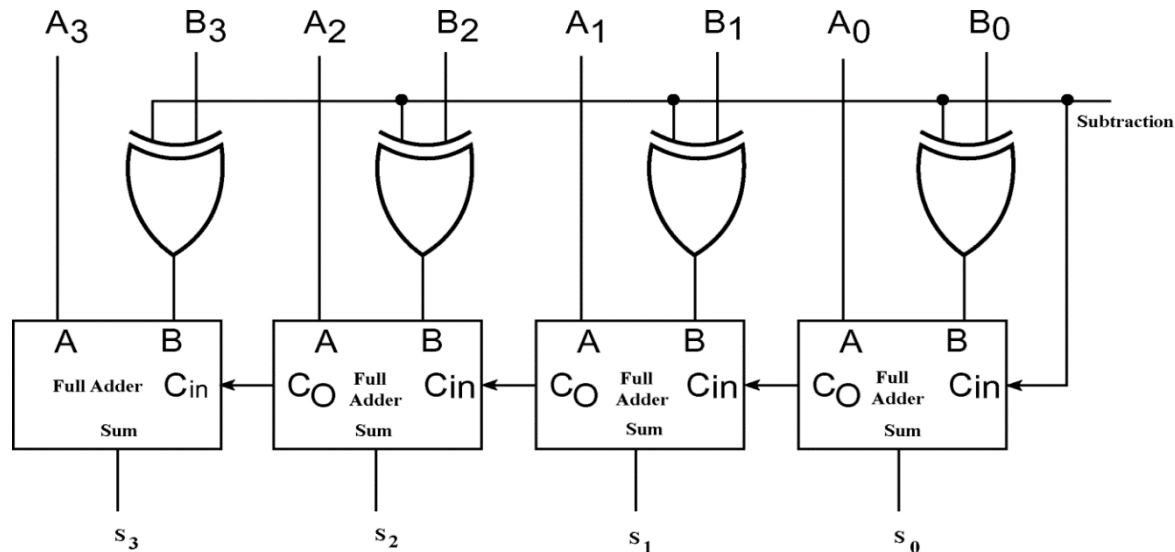



Optimized Multiplier (Fig.3.5)

- Perform steps in parallel: add/shift
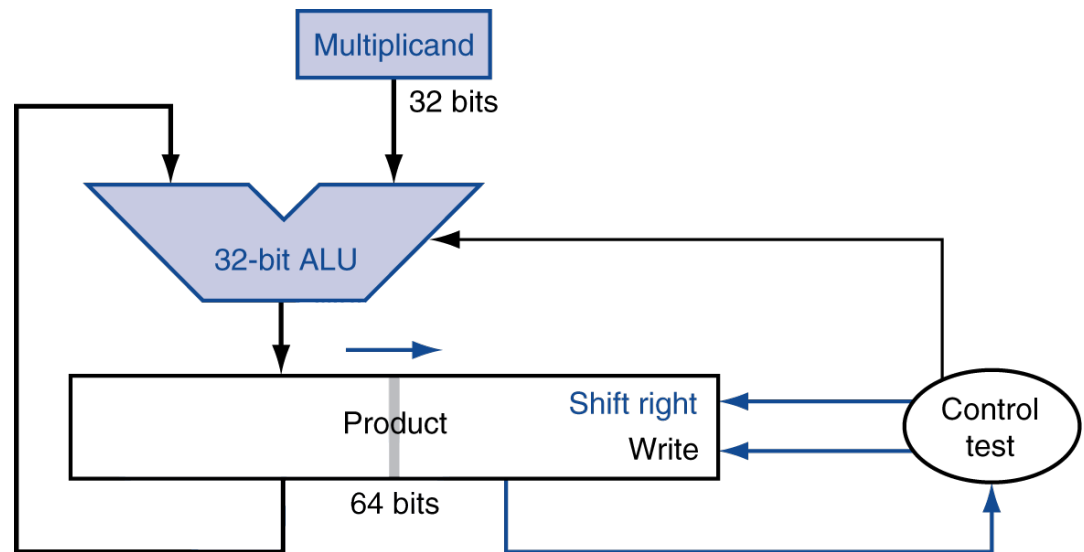
```
  1000
x 1001
=====
  1000
 0000
 0000
+1000
=====
1001000
```



Optimized Divider (Fig. 3.11)

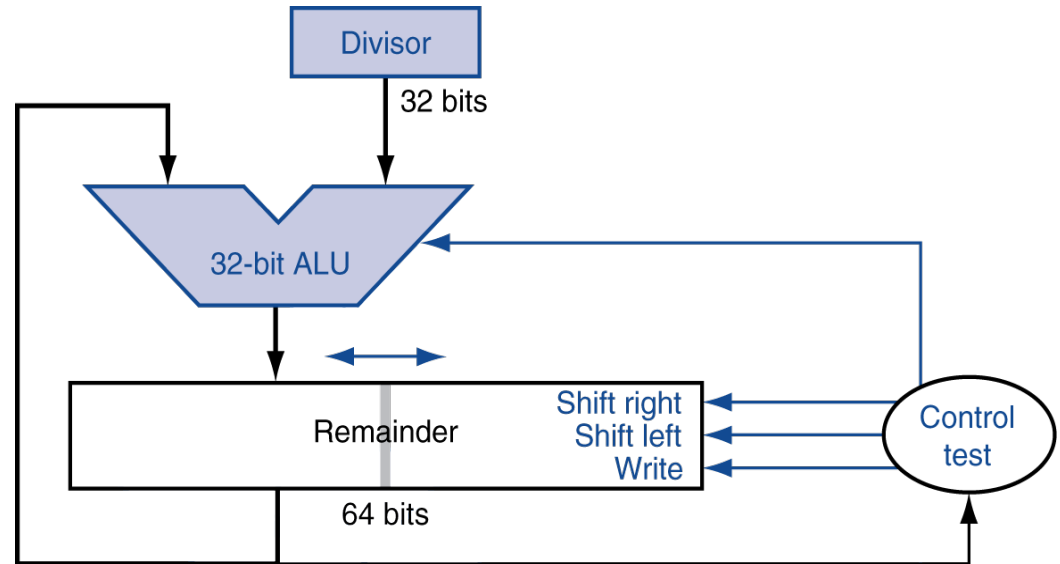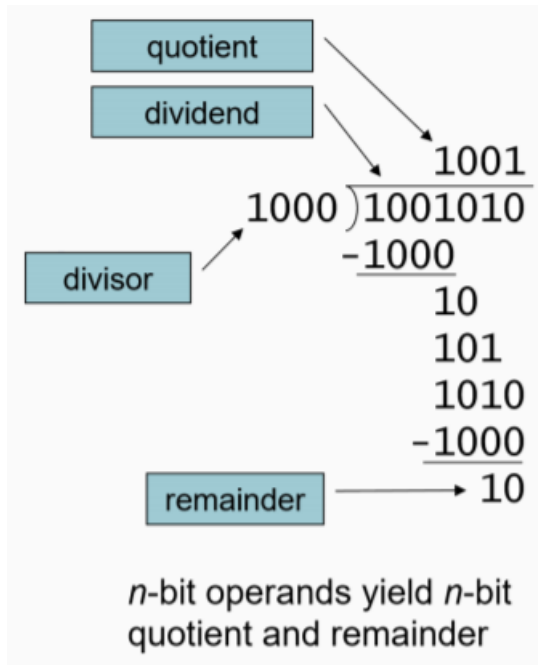

- Looks a lot like a multiplier!
 - Same hardware can be used for both

Floating Point

- Representation for non-integral numbers
 - Including very small and very large numbers
- Like scientific notation
 - -2.34×10^{56} ← normalized
 - $+0.002 \times 10^{-4}$ ← not normalized
 - $+987.02 \times 10^9$ ← not normalized
- In binary
 - $\pm 1.xxxxxxx_2 \times 2^{yyyy}$
- Types `float` and `double` in C

Floating Point Standard

- Defined by **IEEE Std 754-1985**
- Developed in response to divergence of representations
 - Portability issues for scientific code
- Now almost universally adopted
- Two representations
 - Single precision (32-bit)
 - Double precision (64-bit)
- Precision vs. range

IEEE Floating-Point Format

single: 8 bits
double: 11 bits

single: 23 bits
double: 52 bits

S	Exponent	Fraction
---	----------	----------

$$x = (-1)^S \times (1 + \text{Fraction}) \times 2^{(\text{Exponent} - \text{Bias})}$$

- S: sign bit (0 \Rightarrow non-negative, 1 \Rightarrow negative)
- Exponent: excess representation: actual exponent + Bias
 - Ensures exponent is unsigned
 - Single: Bias = 127; Double: Bias = 1203

Subword Parallelism

- Graphics and audio applications can take advantage of performing simultaneous operations on short vectors
 - Example: 128-bit adder:
 - Sixteen 8-bit adds
 - Eight 16-bit adds
 - Four 32-bit adds
- Also called data-level parallelism, vector parallelism, or
- Single Instruction, Multiple Data (SIMD)

x86 FP Architecture

- Originally based on **8087 FP coprocessor**
 - 8×80 -bit extended-precision registers
 - Used as a push-down stack
 - Registers indexed from TOS: ST(0), ST(1), ...
- Very difficult to generate and optimize code
 - Result : poor FP performance

Streaming SIMD Extension 2 (SSE2)

- Can be used for multiple FP operands
 - 2×64 -bit double precision
 - 4×32 -bit double precision
 - Single-Instruction Multiple-Data

Concluding Remarks

- ISAs support arithmetic
 - Signed and unsigned integers
 - Floating-point approximation to reals
- Bounded range and precision
 - Operations can overflow and underflow
- MIPS ISA
 - Core instructions : 54 most frequently used
 - 100% of SPECINT, 97% of SPECFP
 - Other instructions: less frequent

Chap. 4 The Processor


Part A – Simple Implementation

Introduction	244	
Logic Design Conventions	248	
Building a Datapath	251	
A Simple Implementation Scheme	259	
An Overview of Pipelining	272	
Pipelined Datapath and Control	286	
Data Hazards: Forwarding versus Stalling	303	
Control Hazards	316	
Exceptions	325	
Parallelism via Instructions	332	
Real Stuff: The ARM Cortex-A8 and Intel Core i7 Pipelines	344	
Going Faster: Instruction-Level Parallelism and Matrix Multiply	351	
Advanced Topic: An Introduction to Digital Design Using a Hardware Design Language to Describe and Model a Pipeline and More Pipelining Illustrations	354	
Fallacies and Pitfalls	355	
Concluding Remarks	356	
Historical Perspective and Further Reading	357	
Exercises	357	

** NUS, Aaron Tan 교수의 강의자료를 일부 포함하고 있습니다. **



Instruction Execution Cycle (Basic)

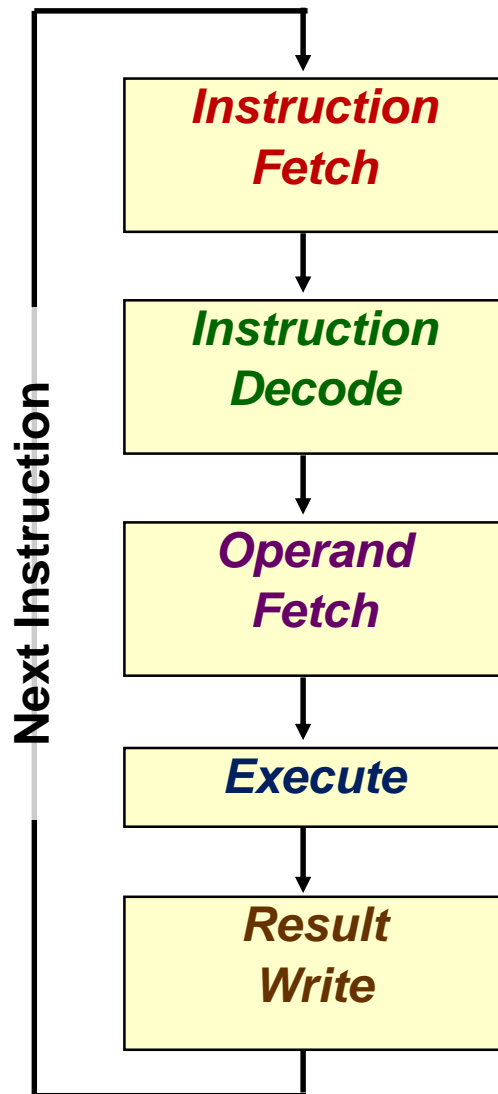

Fetch:

- Get instruction from memory
- Address is in **P**rogram **C**ounter (PC) Register

Decode:

- Find out the operation required

Operand Fetch:

- Get operand(s) needed for operation

Execute:

- Perform the required operation

Result Write (Store):

- Store the result of the operation



The Processor


❑ 2 Major Components for a processor

● Datapath

- Performs the arithmetic, logical and memory operations
- Collection of components that process data
Arithmetic Logic Unit(ALU),
Shifters, Registers, multipliers

● Control

 - Tells the datapath, memory and I/O devices what to do according to program instructions




The Processor (Datapath & Control) Implementation

- ❑ Our implementation of the MIPS is simplified
 - arithmetic and logical instructions: **add, sub, and, or, slt**
 - memory-reference instructions: **lw, sw**
 - control flow instructions: **beq, bne, j**

- ❑ Generic implementation

 - use the PC to supply the instruction address and fetch the instruction from memory (and update the PC)
- decode the instruction (and read registers)
- execute the instruction



- ❑ All instructions (except **j**) use the ALU after reading the registers
 - *Arithmetic result : add, addi, sub, and, or*
 - *Memory address for load/store*
 - *Comparison result for branches*



Clocking Methodologies

- ❑ The **clocking methodology** defines when data in a state element is valid and stable relative to the clock
 - State elements - a memory element such as a register
 - Edge triggered - all state changes occur on a clock edge

- ❑ Typical execution
 - read contents of state elements
 - send values through combinational logic
 - write results to one or more state elements




Register Transfer Language and Clocking

Register transfer in RTL:

$$R2 \leftarrow f(R1)$$

What Really Happens Physically

 

Two possible clocking methodologies : positively triggered or negatively triggered. This class uses the negatively-triggered.



Building a Datapath

- MIPS Instruction Execution
- Design changes:
 - Merge *Decode* and *Operand Fetch* – Decode is simple for MIPS
 - Split *Execute* into **ALU** (Calculation) and **Memory Access**

	<code>add \$3, \$1, \$2</code>	<code>lw \$3, 20(\$1)</code>	<code>beq \$1, \$2, label</code>
Fetch	Read inst. at [PC]	Read inst. at [PC]	Read inst. at [PC]
Decode & Operand Fetch	<ul style="list-style-type: none"> ○ Read [\$1] as <i>opr1</i> ○ Read [\$2] as <i>opr2</i> 	<ul style="list-style-type: none"> ○ Read [\$1] as <i>opr1</i> ○ Use 20 as <i>opr2</i> 	<ul style="list-style-type: none"> ○ Read [\$1] as <i>opr1</i> ○ Read [\$2] as <i>opr2</i>
ALU	$Result = opr1 + opr2$	$MemAddr = opr1 + opr2$	$Taken = (opr1 == opr2) ?$ $Target = (PC+4) + ofst \times 4$
Memory Access		Use <i>MemAddr</i> to read from memory	
Result Write	<i>Result</i> stored in \$3	<i>Memory data</i> stored in \$3	if (<i>Taken</i>) $PC = Target$


opr = operand **MemAddr** = Memory Address **ofst** = offset



Fetching Instructions

❑ Fetching instructions involves

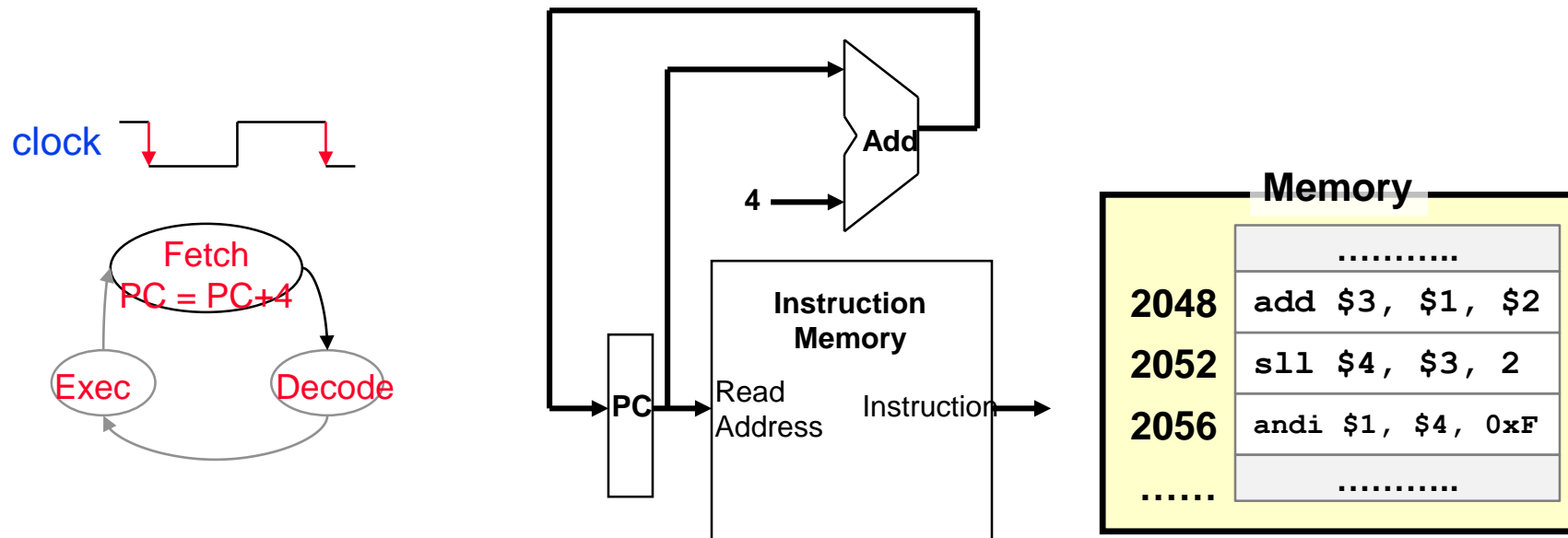- reading the instruction from the Instruction Memory
- updating the PC value to be the address of the next (sequential) instruction




- PC is updated every clock cycle, so it does not need an explicit write control signal just a clock signal
- Reading from the Instruction Memory is a combinational activity, so it doesn't need an explicit read control signal



Decoding Instructions

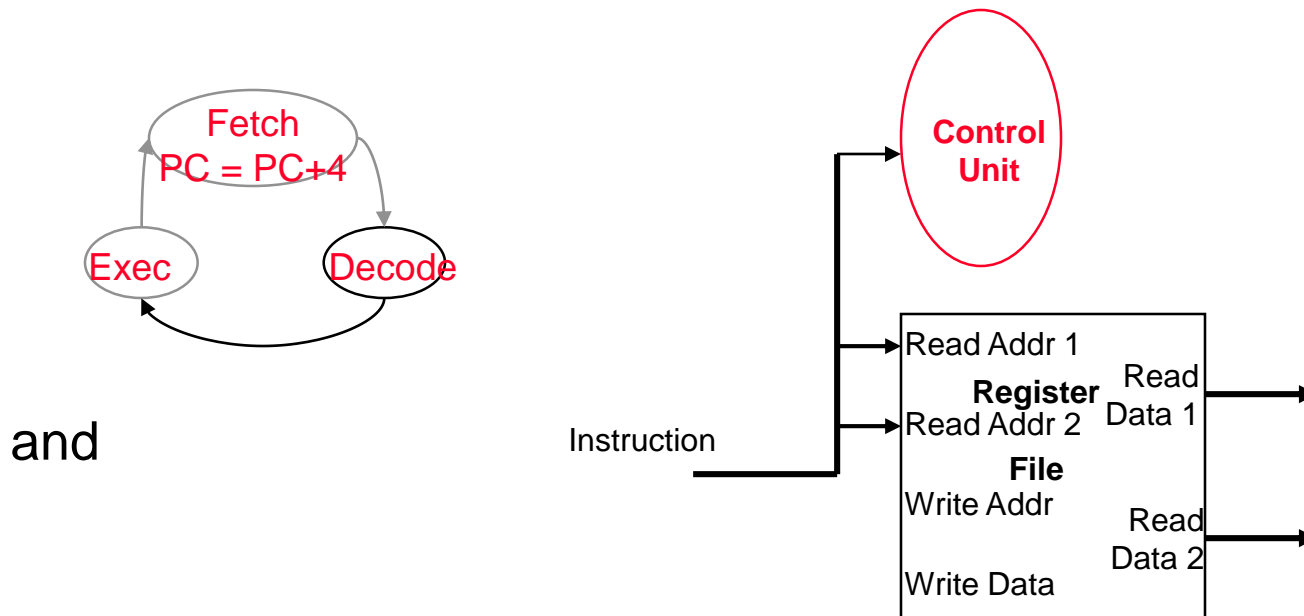
- ❑ Decoding instructions involves
 - sending the fetched instruction's opcode and function field bits to the control unit



- reading two values from the Register File
 - Register File addresses are contained in the instruction




Decode Stage: R-Format Instruction

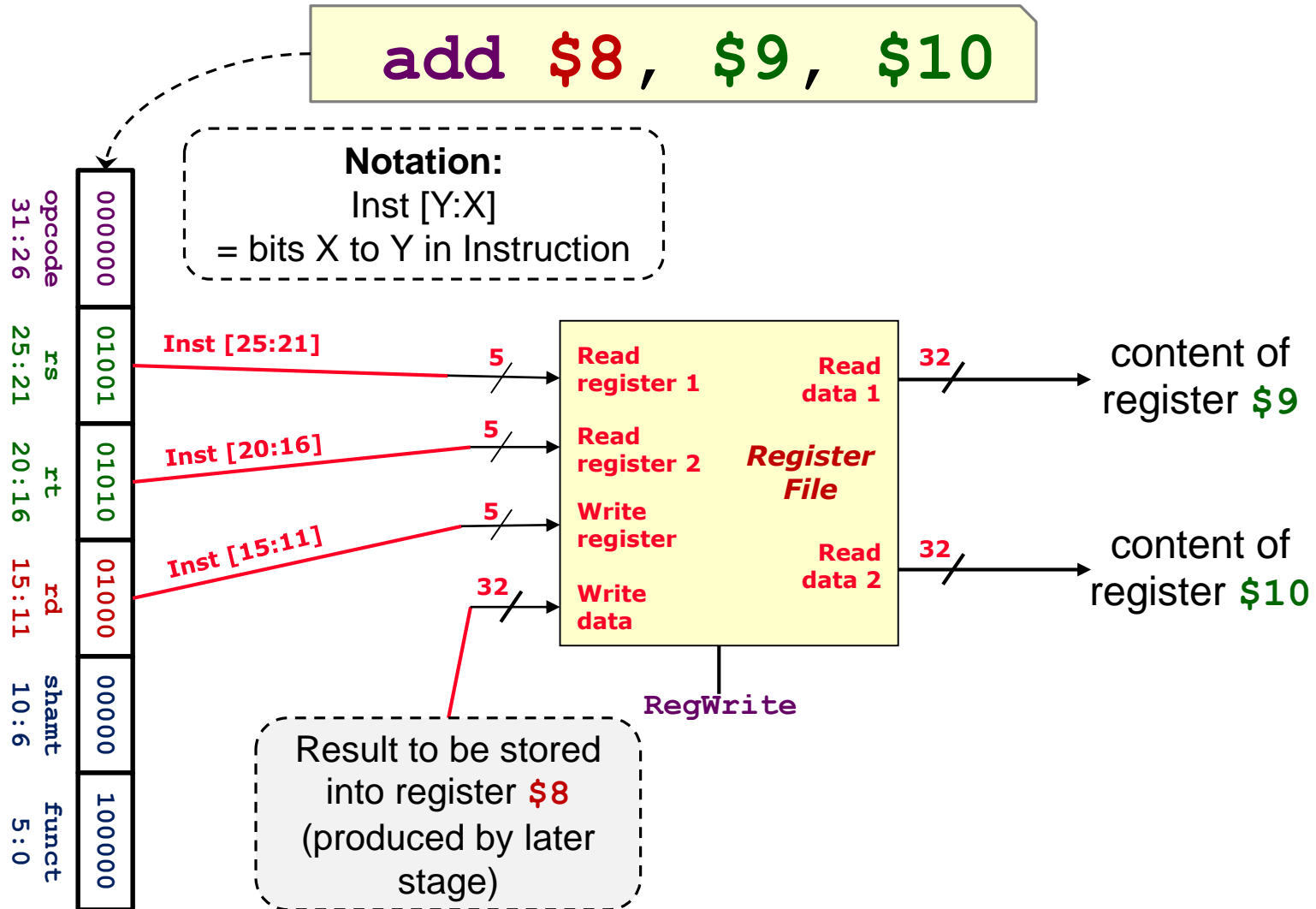


Decode Stage: Load Word Instruction

lw \$21, -50(\$22)

 


Decode Stage: Branch Instruction

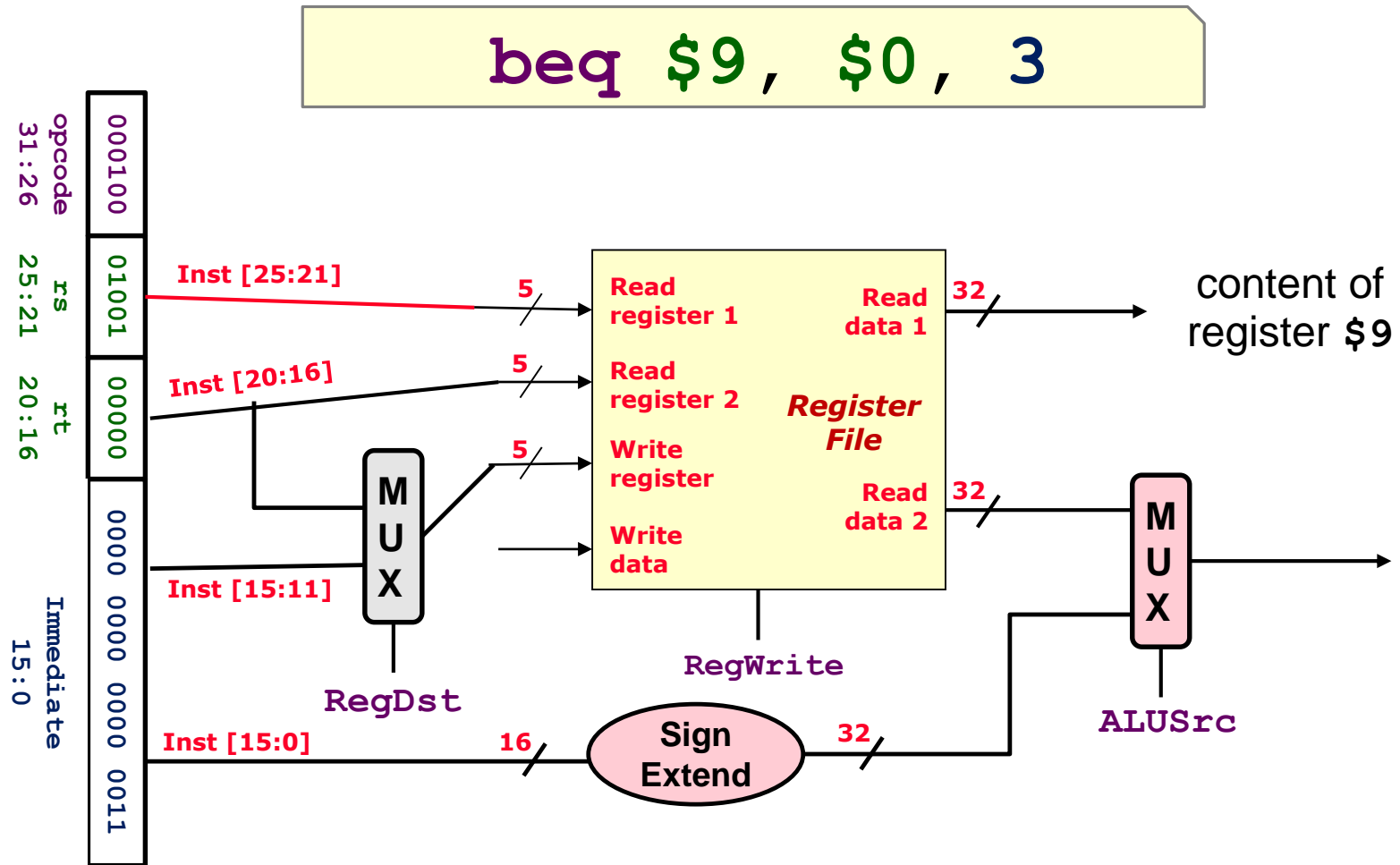


Executing R Format Operations

 □ R format operations (**add**, **sub**, **slt**, **and**, **or**)



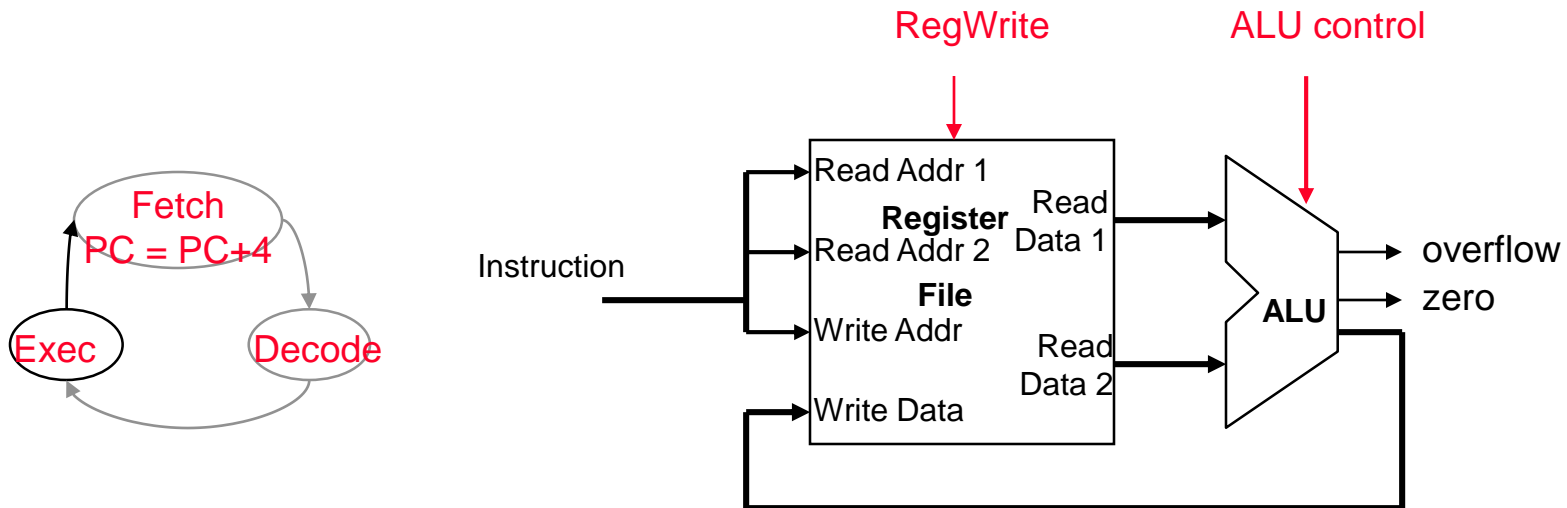- perform operation (**op** and **funct**) on values in **rs** and **rt**
- store the result back into the Register File (into location **rd**)




- Note that Register File is not written every cycle (e.g. **sw**), so we need an explicit write control signal for the Register File

Executing Load and Store Operations

□ Load and store operations involves

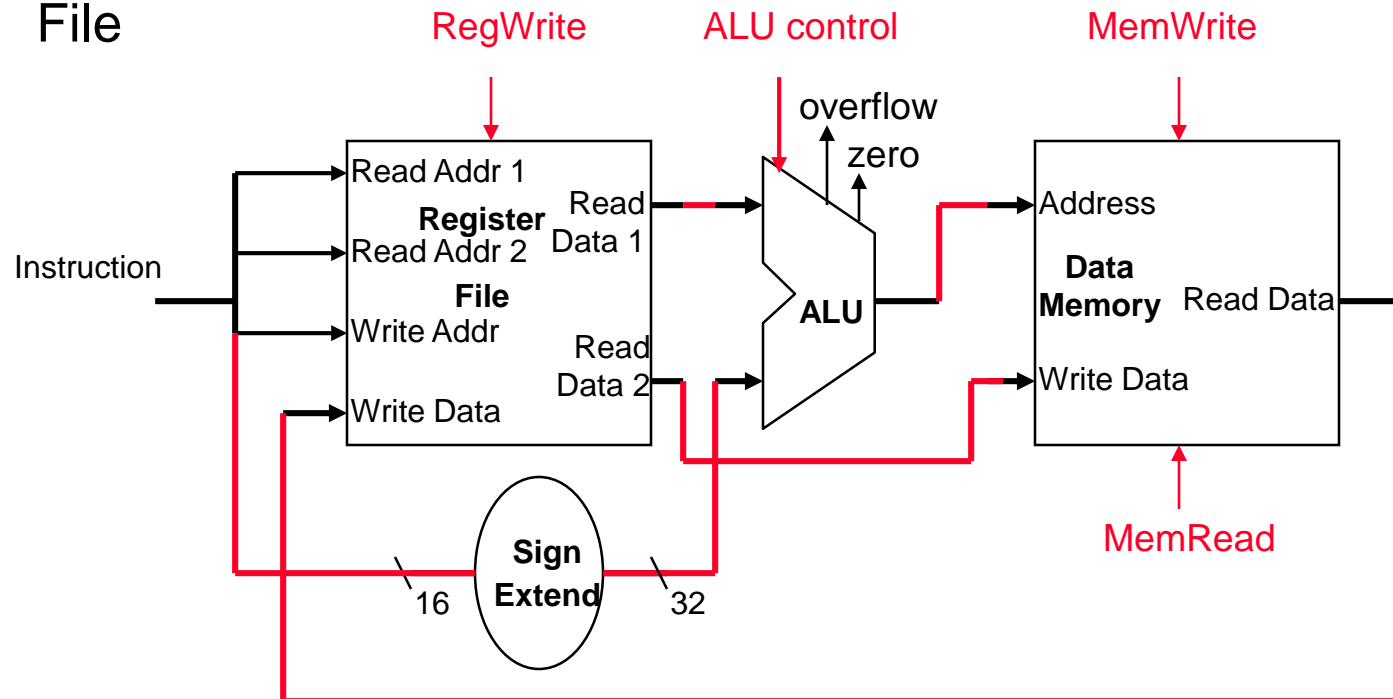
- **compute memory address** by adding the base register (read from the Register File during decode) to the 16-bit signed-extended offset field in the instruction
- **store** value (read from the Register File during decode) written to the Data Memory
- **load** value, read from the Data Memory, written to the Register File



Executing Branch Operations

❑ Branch operations involves

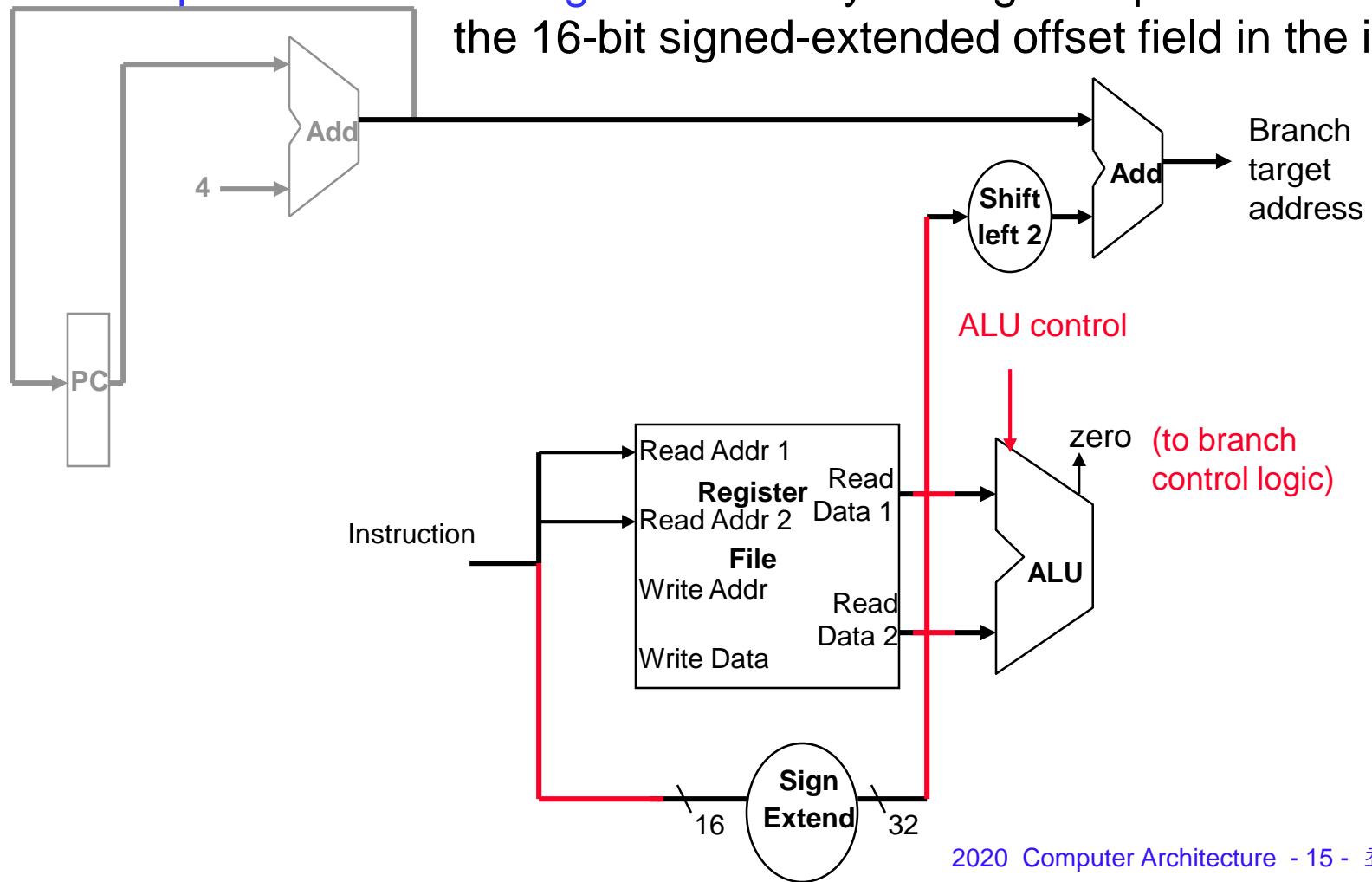- compare the operands read from the Register File during decode for equality (**zero** ALU output)
- compute the branch target address by adding the updated PC to the 16-bit signed-extended offset field in the instr



Creating a Single Datapath from the Parts

- ❑ Assemble the datapath segments and add control lines and multiplexors as needed
- ❑ **Single cycle** design – fetch, decode and execute each instructions in **one** clock cycle
 - no datapath resource can be used more than once per instruction, so some must be duplicated (e.g., separate Instruction Memory and Data Memory, several adders)
 - **multiplexors** needed at the input of shared elements with control lines to do the selection
 - write signals to control writing to the Register File and Data Memory
- ❑ Cycle time is determined by length of the longest path



Fetch, R, and Memory Access Portions

