

---


# Chap. 4 The Processor

## Part A – Simple Implementation

<b>Introduction</b>	244	
<b>Logic Design Conventions</b>	248	
<b>Building a Datapath</b>	251	
<b>A Simple Implementation Scheme</b>	259	
<b>An Overview of Pipelining</b>	272	
<b>Pipelined Datapath and Control</b>	286	
<b>Data Hazards: Forwarding versus Stalling</b>	303	
<b>Control Hazards</b>	316	
<b>Exceptions</b>	325	
<b>Parallelism via Instructions</b>	332	
<b>Real Stuff: The ARM Cortex-A8 and Intel Core i7 Pipelines</b>	344	
<b>Going Faster: Instruction-Level Parallelism and Matrix Multiply</b>	351	
<b>Advanced Topic: An Introduction to Digital Design Using a Hardware Design Language to Describe and Model a Pipeline and More Pipelining Illustrations</b>	354	
<b>Fallacies and Pitfalls</b>	355	
<b>Concluding Remarks</b>	356	
<b>Historical Perspective and Further Reading</b>	357	
<b>Exercises</b>	357	

*\* NUS, Aaron Tan 교수의 강의자료를 일부 포함하고 있습니다. \**

# Instruction Execution Cycle (Basic)

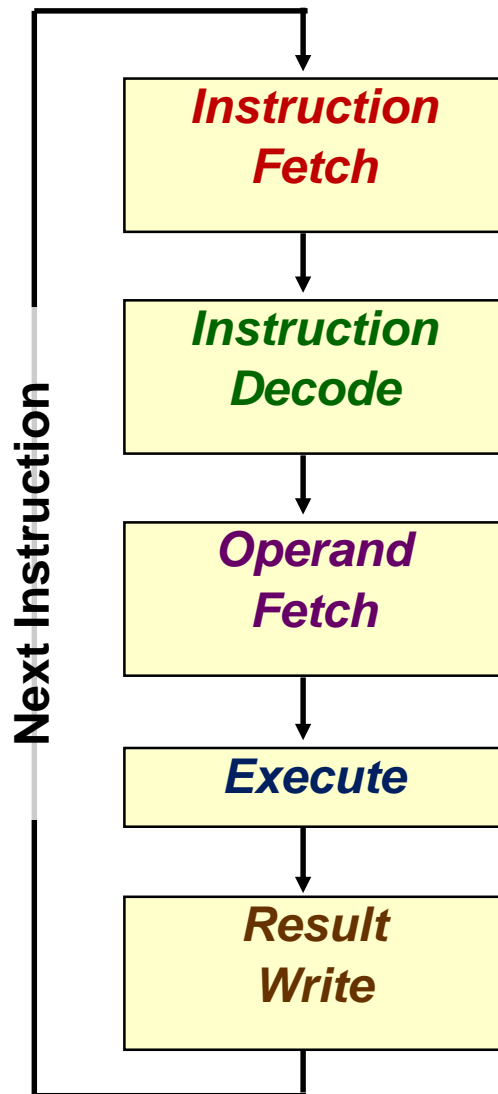

## Fetch:

- Get instruction from memory
- Address is in **P**rogram **C**ounter (PC) Register

## Decode:

- Find out the operation required

## Operand Fetch:

- Get operand(s) needed for operation

## Execute:

- Perform the required operation

## Result Write (Store):

- Store the result of the operation

# The Processor


## ❑ 2 Major Components for a processor

### ● Datapath

- Performs the arithmetic, logical and memory operations
- Collection of components that process data  
Arithmetic Logic Unit(ALU), Shifters, Registers, multipliers
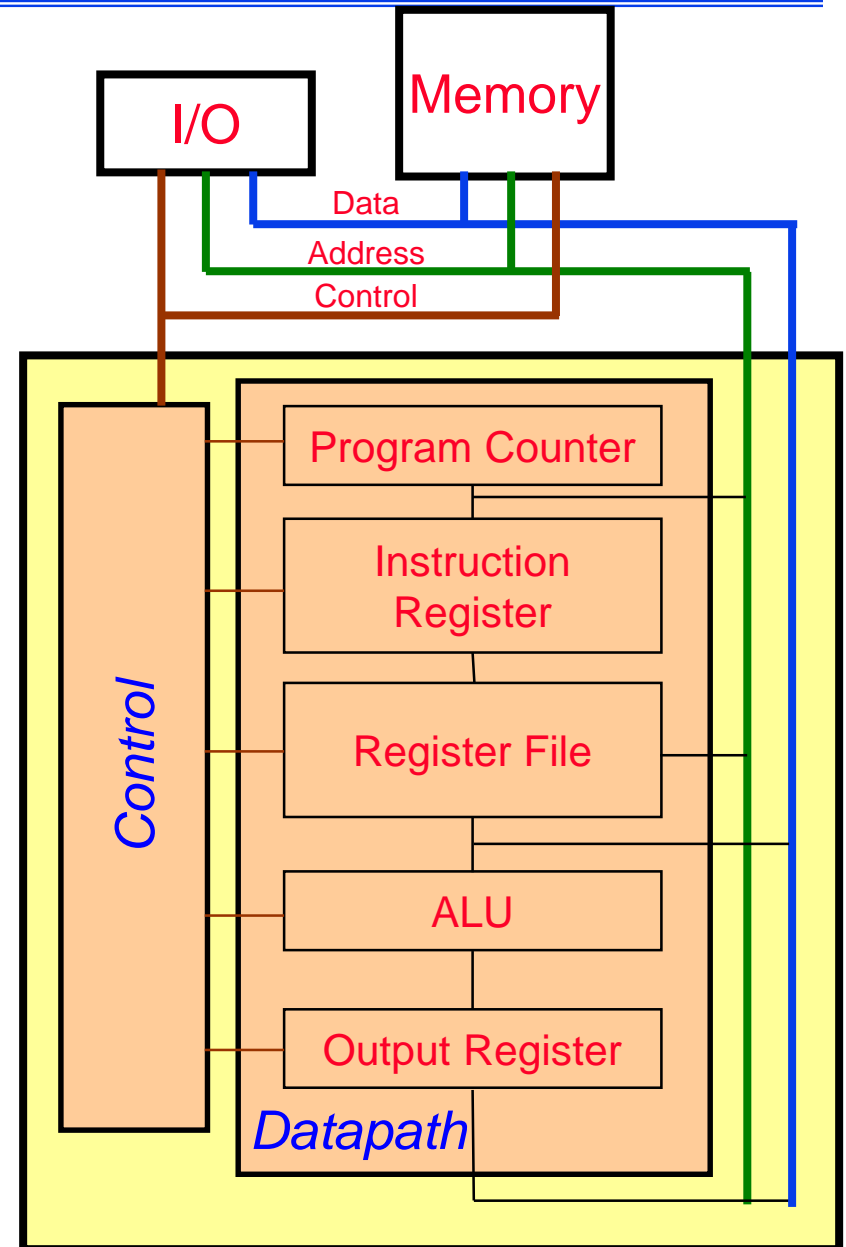
### ● Control

- Tells the datapath, memory and I/O devices what to do according to program instructions




# The Processor (Datapath & Control) Implementation

- ❑ Our implementation of the MIPS is simplified
  - arithmetic and logical instructions: **add, sub, and, or, slt**
  - memory-reference instructions: **lw, sw**
  - control flow instructions: **beq, bne, j**

- ❑ Generic implementation

 - use the PC to supply the instruction address and fetch the instruction from memory (and update the PC)
- decode the instruction (and read registers)
- execute the instruction



- ❑ All instructions (except **j**) use the ALU after reading the registers
  - *Arithmetic result : add, addi, sub, and, or*
  - *Memory address for load/store*
  - *Comparison result for branches*

# Clocking Methodologies

---


- ❑ The **clocking methodology** defines when data in a state element is valid and stable relative to the clock
  - State elements - a memory element such as a register
  - Edge triggered - all state changes occur on a clock edge
  
- ❑ Typical execution
  - read contents of state elements
  - send values through combinational logic
  - write results to one or more state elements

# Register Transfer Language and Clocking

Register transfer in RTL:

$$R2 \leftarrow f(R1)$$

What Really Happens Physically

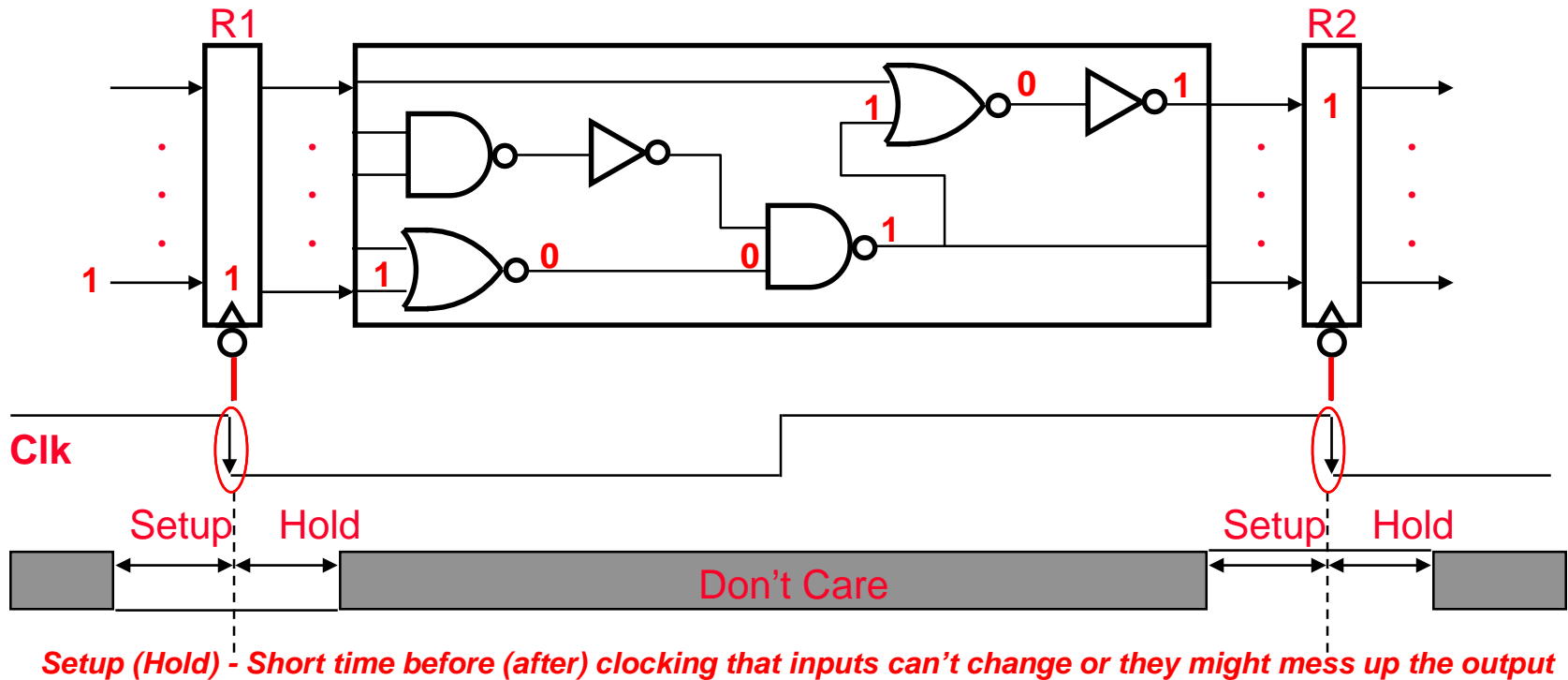

Two possible clocking methodologies : positively triggered or negatively triggered. This class uses the negatively-triggered.

# Building a Datapath

- MIPS Instruction Execution
- Design changes:
  - Merge *Decode* and *Operand Fetch* – Decode is simple for MIPS
  - Split *Execute* into **ALU** (Calculation) and **Memory Access**


	<code>add \$3, \$1, \$2</code>	<code>lw \$3, 20( \$1 )</code>	<code>beq \$1, \$2, label</code>
<b>Fetch</b>	Read inst. at [PC]	Read inst. at [PC]	Read inst. at [PC]
<b>Decode &amp; Operand Fetch</b>	<ul style="list-style-type: none"> <li>○ Read [\$1] as <i>opr1</i></li> <li>○ Read [\$2] as <i>opr2</i></li> </ul>	<ul style="list-style-type: none"> <li>○ Read [\$1] as <i>opr1</i></li> <li>○ Use <b>20</b> as <i>opr2</i></li> </ul>	<ul style="list-style-type: none"> <li>○ Read [\$1] as <i>opr1</i></li> <li>○ Read [\$2] as <i>opr2</i></li> </ul>
<b>ALU</b>	$Result = opr1 + opr2$	$MemAddr = opr1 + opr2$	$Taken = (opr1 == opr2) ?$ $Target = (PC+4) + ofst \times 4$
<b>Memory Access</b>		Use <i>MemAddr</i> to read from memory	
<b>Result Write</b>	<i>Result</i> stored in <b>\$3</b>	<i>Memory data</i> stored in <b>\$3</b>	if ( <i>Taken</i> ) $PC = Target$

**opr** = operand    **MemAddr** = Memory Address    **ofst** = offset

# Fetching Instructions
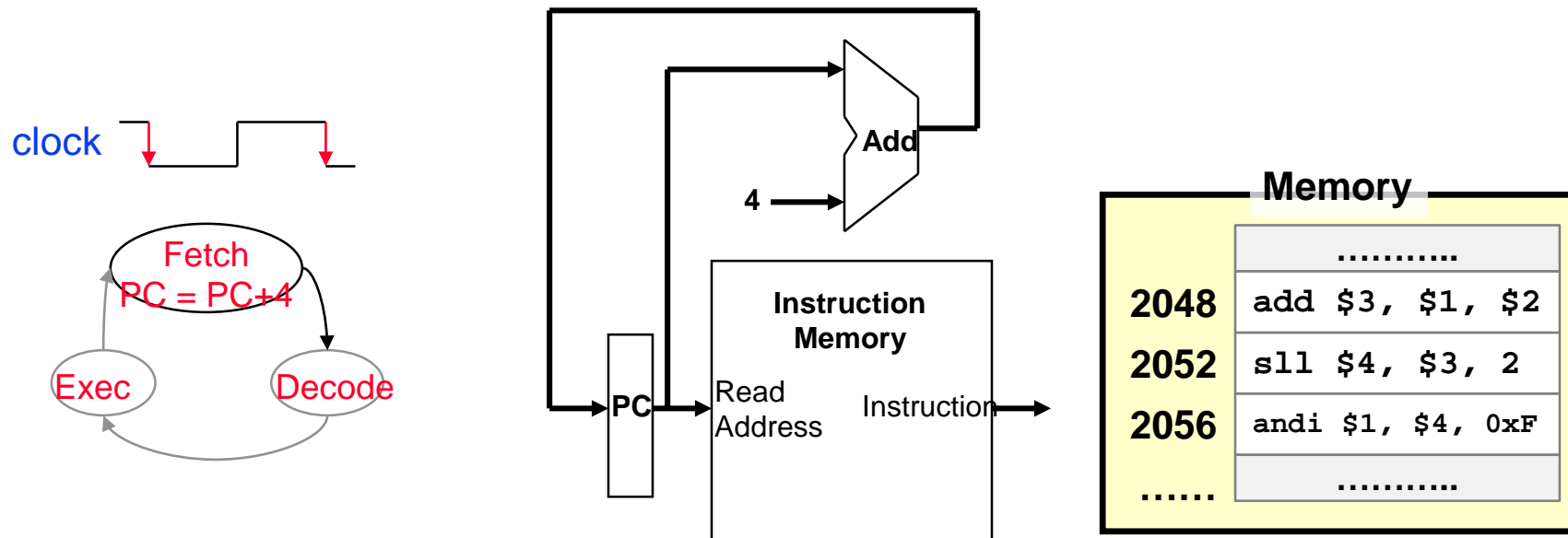
## ❑ Fetching instructions involves

- reading the instruction from the Instruction Memory
- updating the PC value to be the address of the next (sequential) instruction




- PC is updated every clock cycle, so it does not need an explicit write control signal just a clock signal
- Reading from the Instruction Memory is a combinational activity, so it doesn't need an explicit read control signal



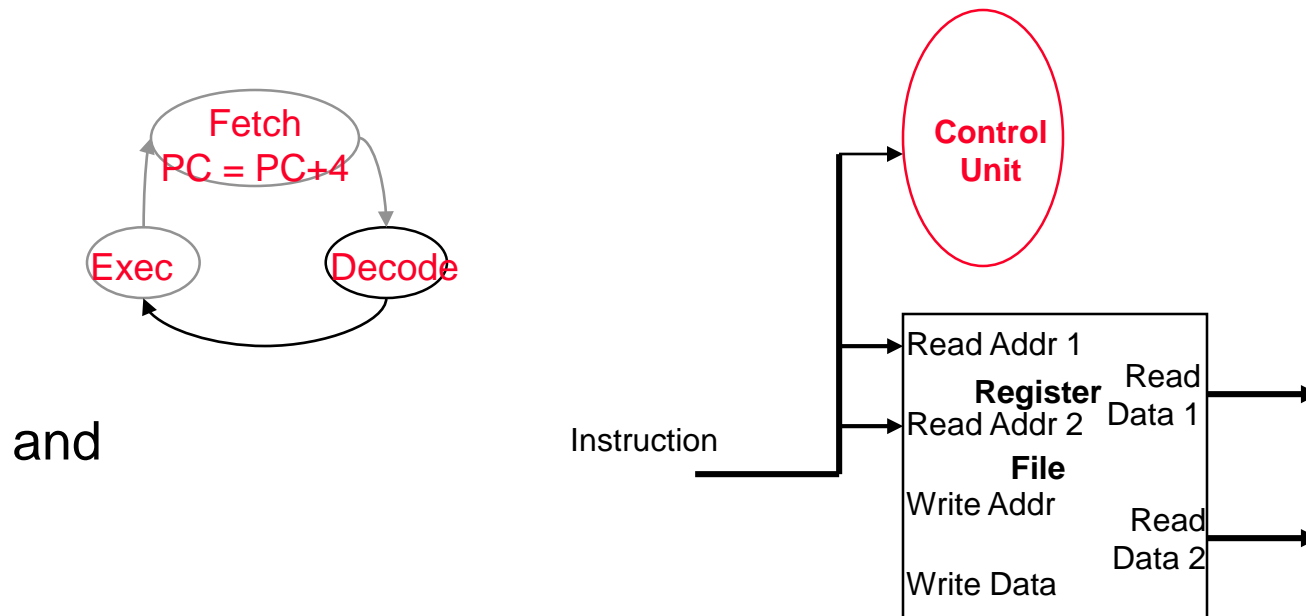
# Decoding Instructions

- ❑ Decoding instructions involves
  - sending the fetched instruction's opcode and function field bits to the control unit




- reading two values from the Register File
  - Register File addresses are contained in the instruction

# Decode Stage: R-Format Instruction

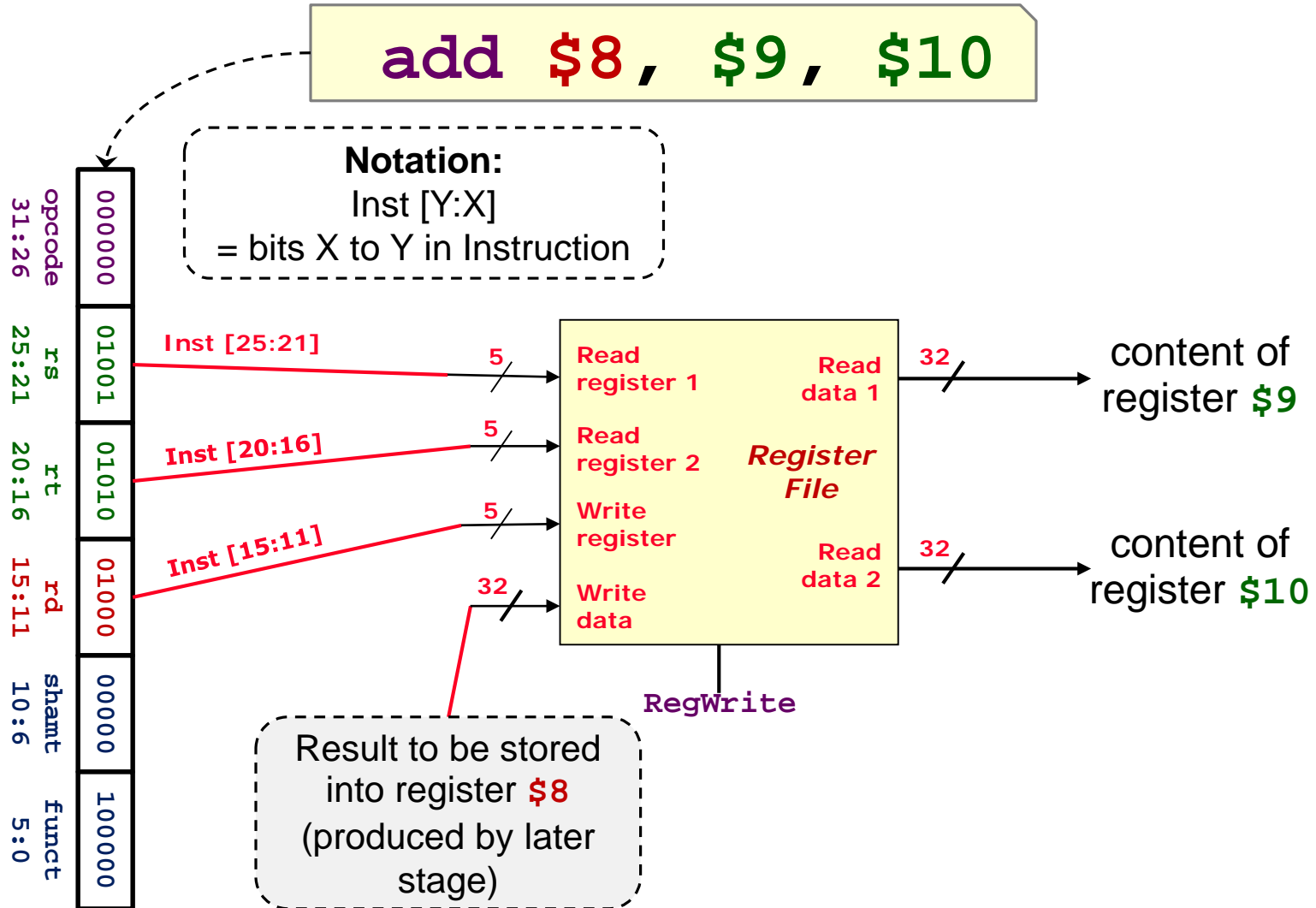


# Decode Stage: Load Word Instruction

**lw \$21, -50(\$22)**

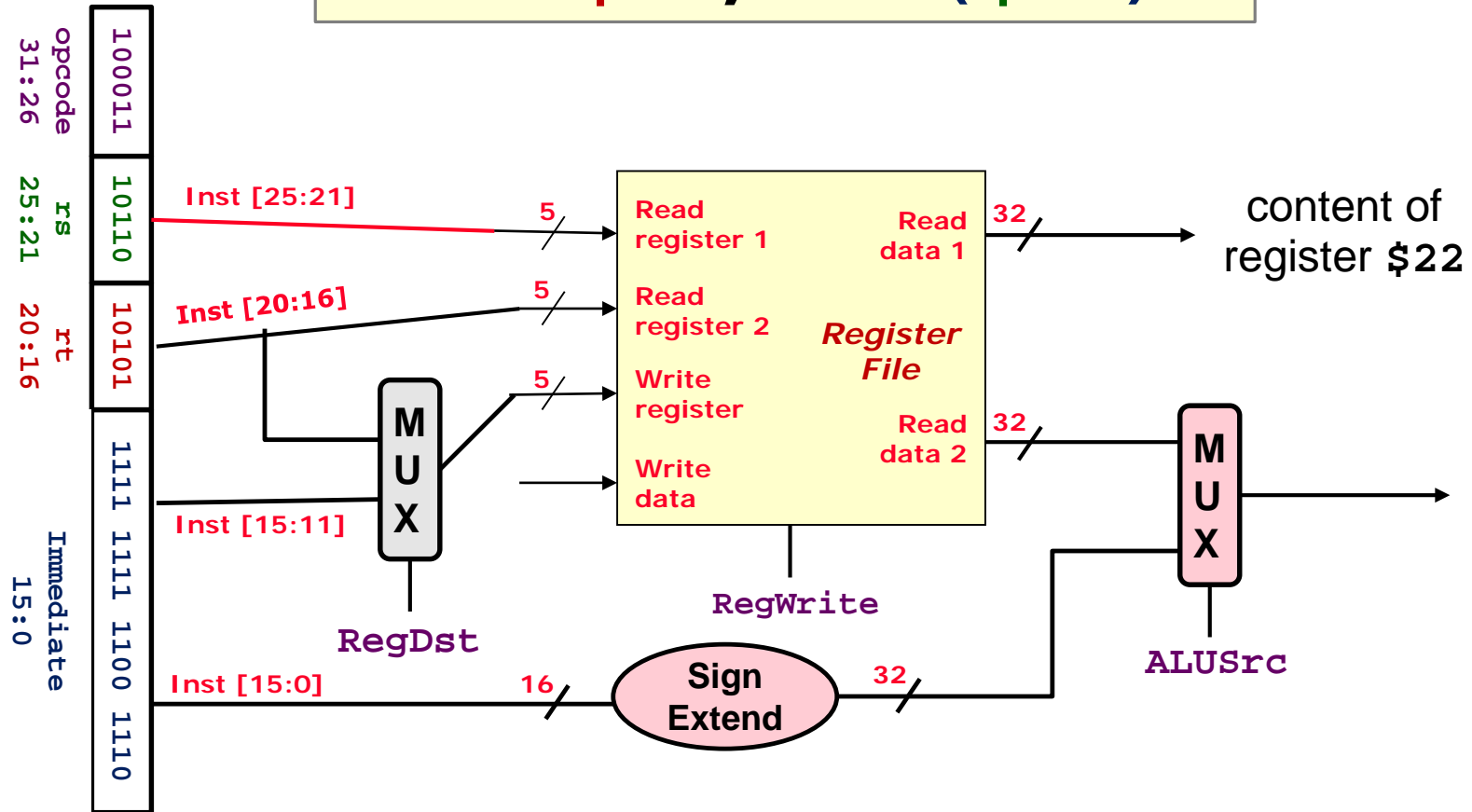


# Decode Stage: Branch Instruction


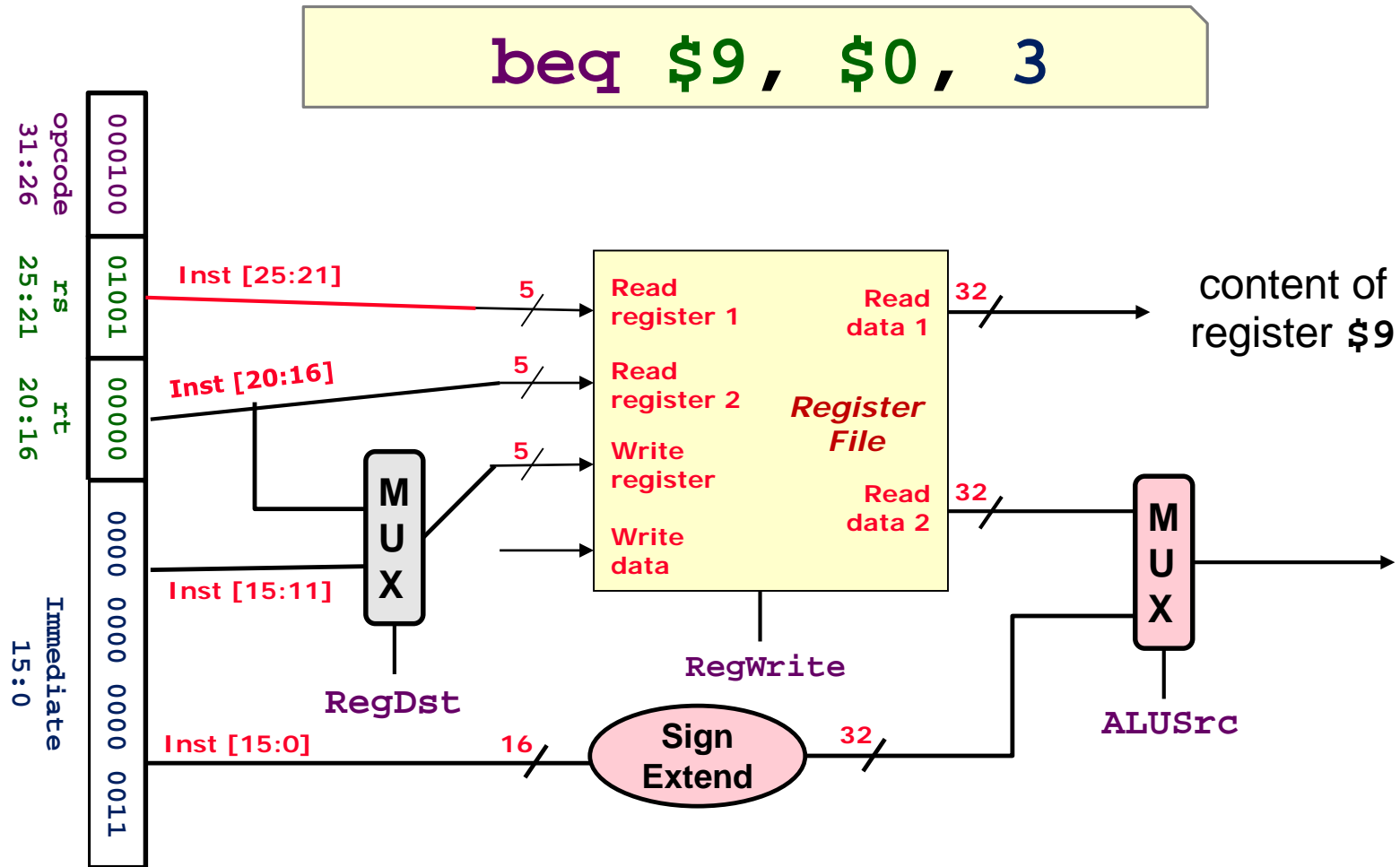

 
# Executing R Format Operations

□ R format operations (**add**, **sub**, **slt**, **and**, **or**)



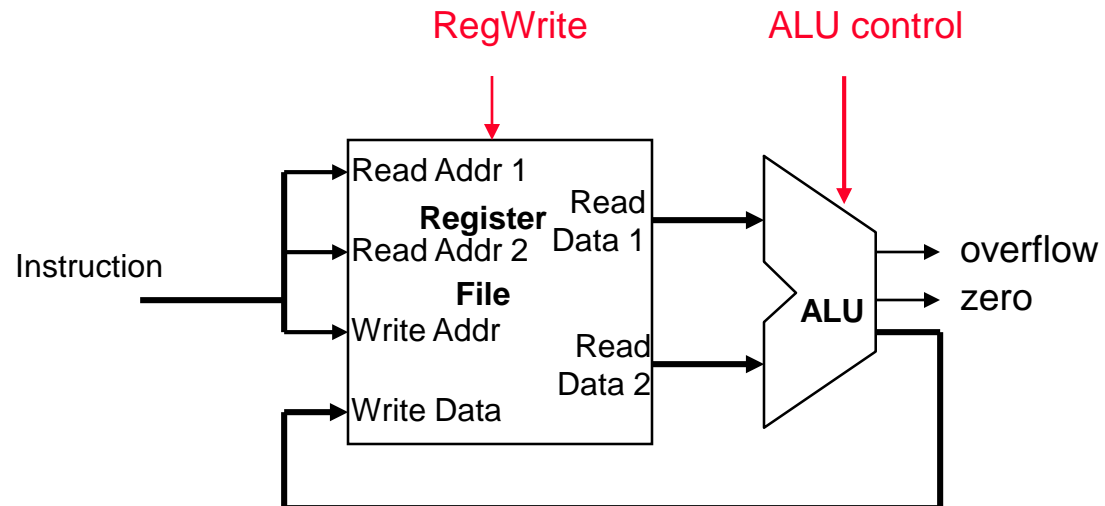 
- perform operation (**op** and **funct**) on values in **rs** and **rt**
- store the result back into the Register File (into location **rd**)



- Note that Register File is not written every cycle (e.g. **sw**), so we need an explicit write control signal for the Register File
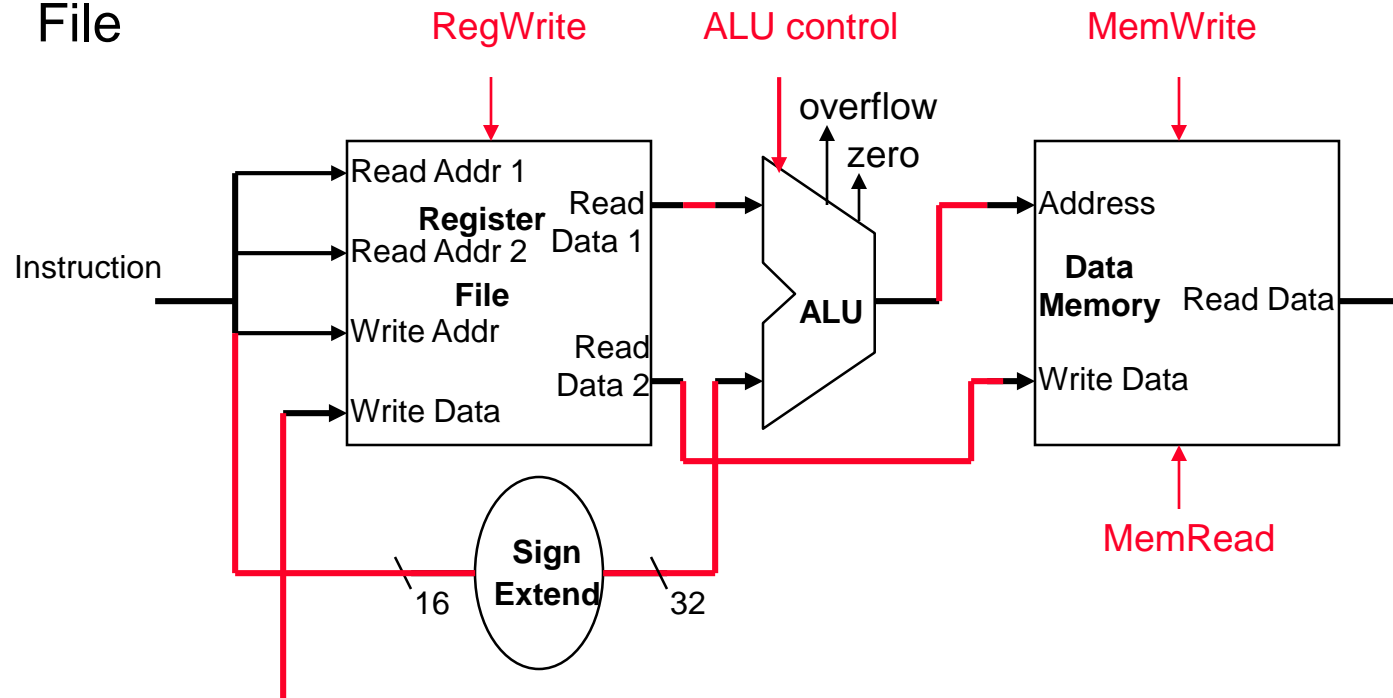
# Executing Load and Store Operations


- ❑ Load and store operations involves
  - **compute memory address** by adding the base register (read from the Register File during decode) to the 16-bit signed-extended offset field in the instruction
  - **store** value (read from the Register File during decode) written to the Data Memory
  - **load** value, read from the Data Memory, written to the Register File



# Executing Branch Operations
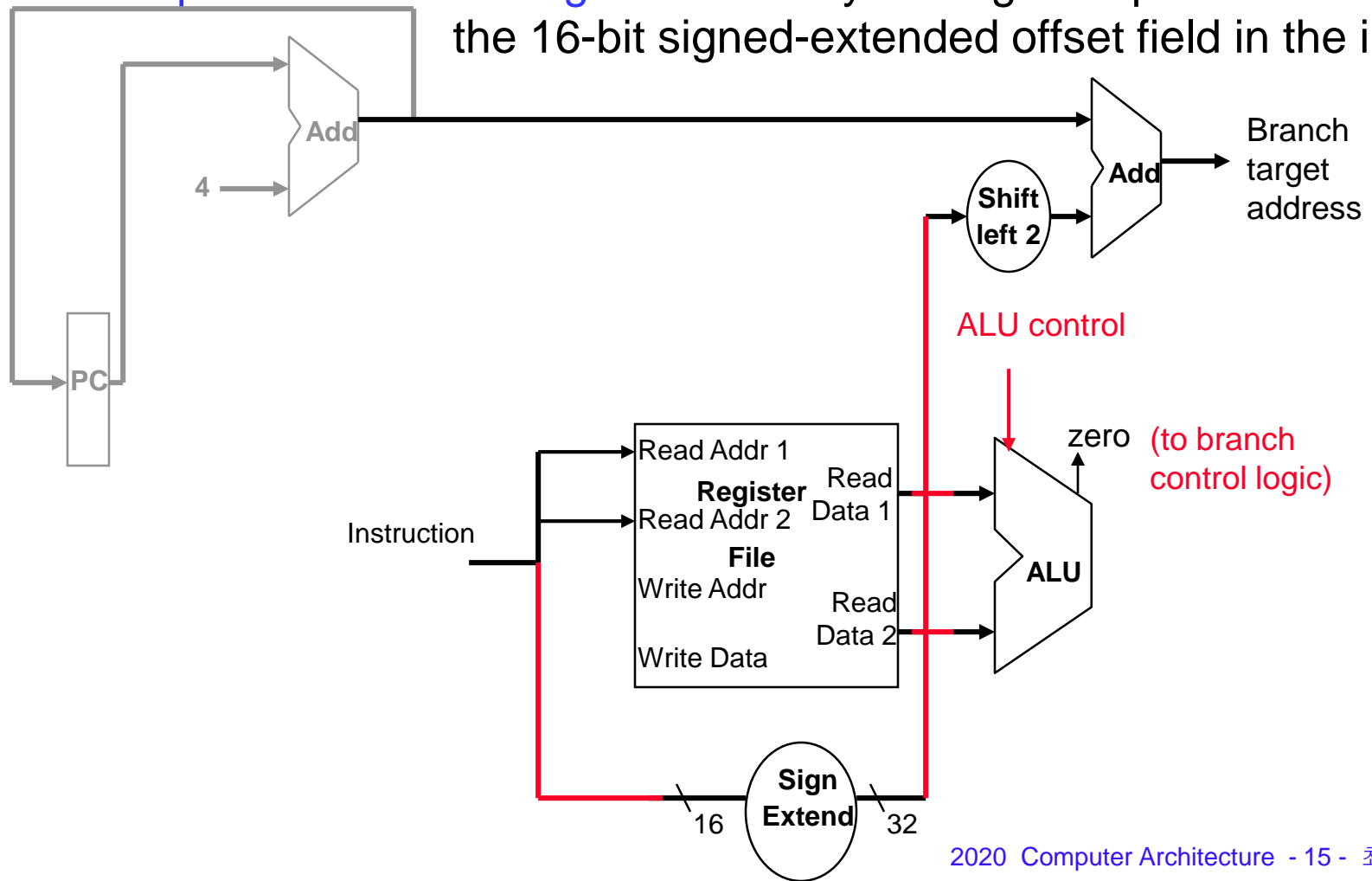
## ❑ Branch operations involves

- compare the operands read from the Register File during decode for equality (**zero** ALU output)
- compute the branch target address by adding the updated PC to the 16-bit signed-extended offset field in the instr




# Creating a Single Datapath from the Parts

- ❑ Assemble the datapath segments and add control lines and multiplexors as needed
  
- ❑ **Single cycle** design – fetch, decode and execute each instructions in **one** clock cycle
  - no datapath resource can be used more than once per instruction, so some must be duplicated (e.g., separate Instruction Memory and Data Memory, several adders)
  - **multiplexors** needed at the input of shared elements with control lines to do the selection
  - write signals to control writing to the Register File and Data Memory
  
- ❑ Cycle time is determined by length of the longest path



# Fetch, R, and Memory Access Portions

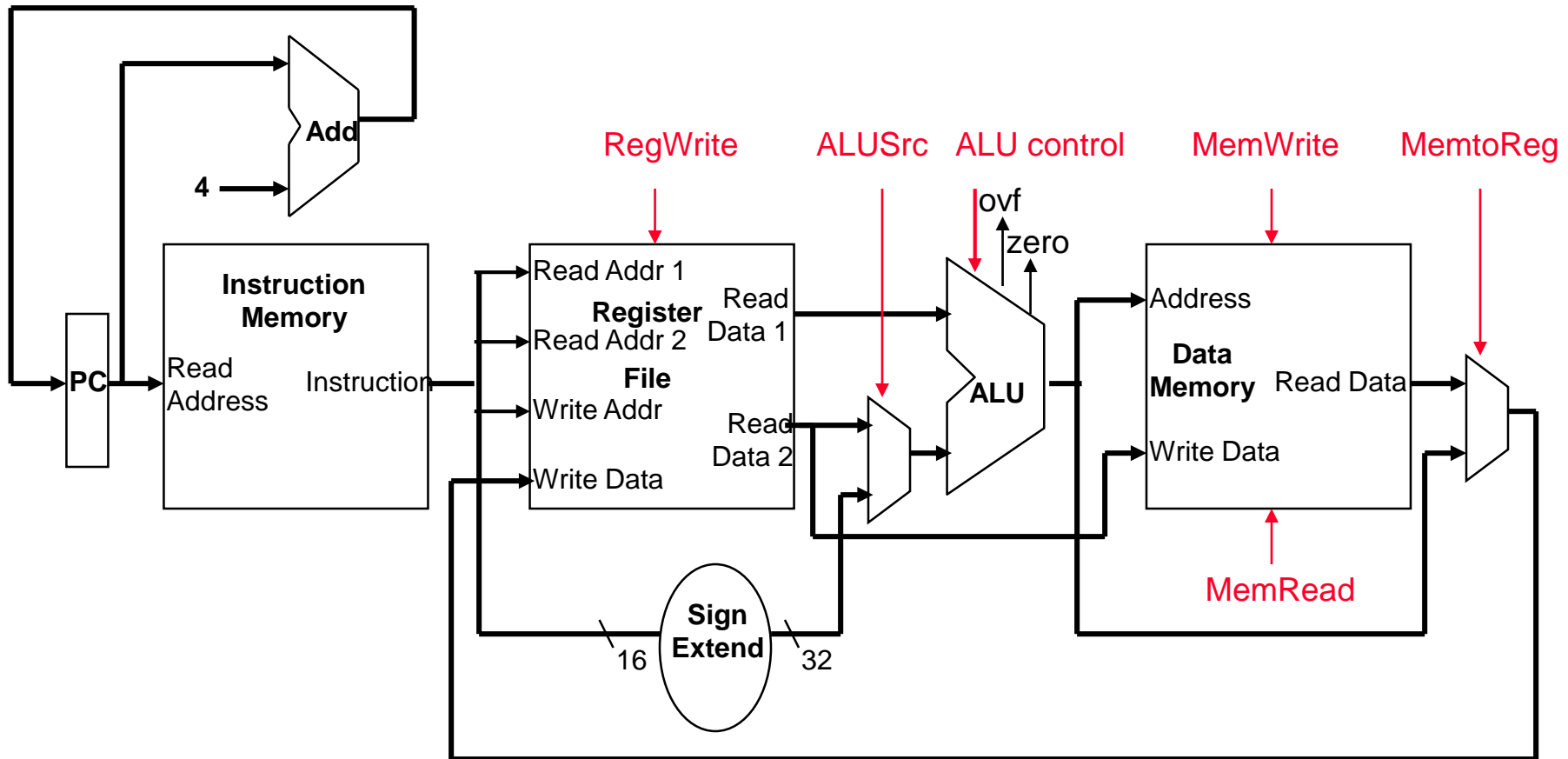

---

## □ Summary


- Single cycle datapath

# Adding the Control

Selecting the operations to perform


- ALU
- Register File
- and Memory read/write

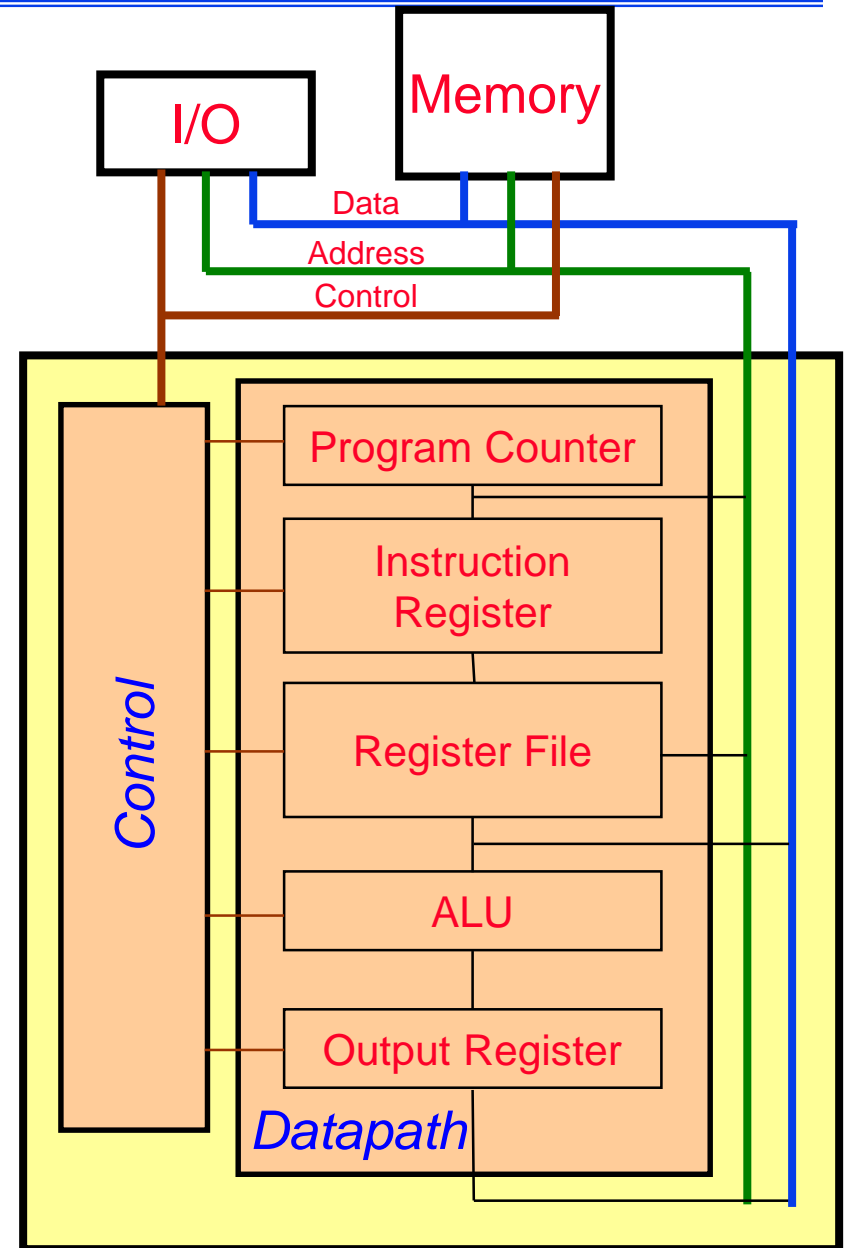Controlling the flow of data (multiplexor inputs)


 
# Adding the Control


- ❑ Selecting the operations to perform (ALU, Register File and Memory read/write)
- ❑ Controlling the flow of data (multiplexor inputs)




## ❑ Observations

- op field **always** in bits 31-26
- addr of registers to be read are **always** specified by the rs field (bits 25-21) and rt field (bits 20-16); for lw and sw rs is the base register
- addr. of register to be written is in one of **two** places – in rt (bits 20-16) for lw; in rd (bits 15-11) for R-type instructions
- offset for beq, lw, and sw **always** in bits 15-0

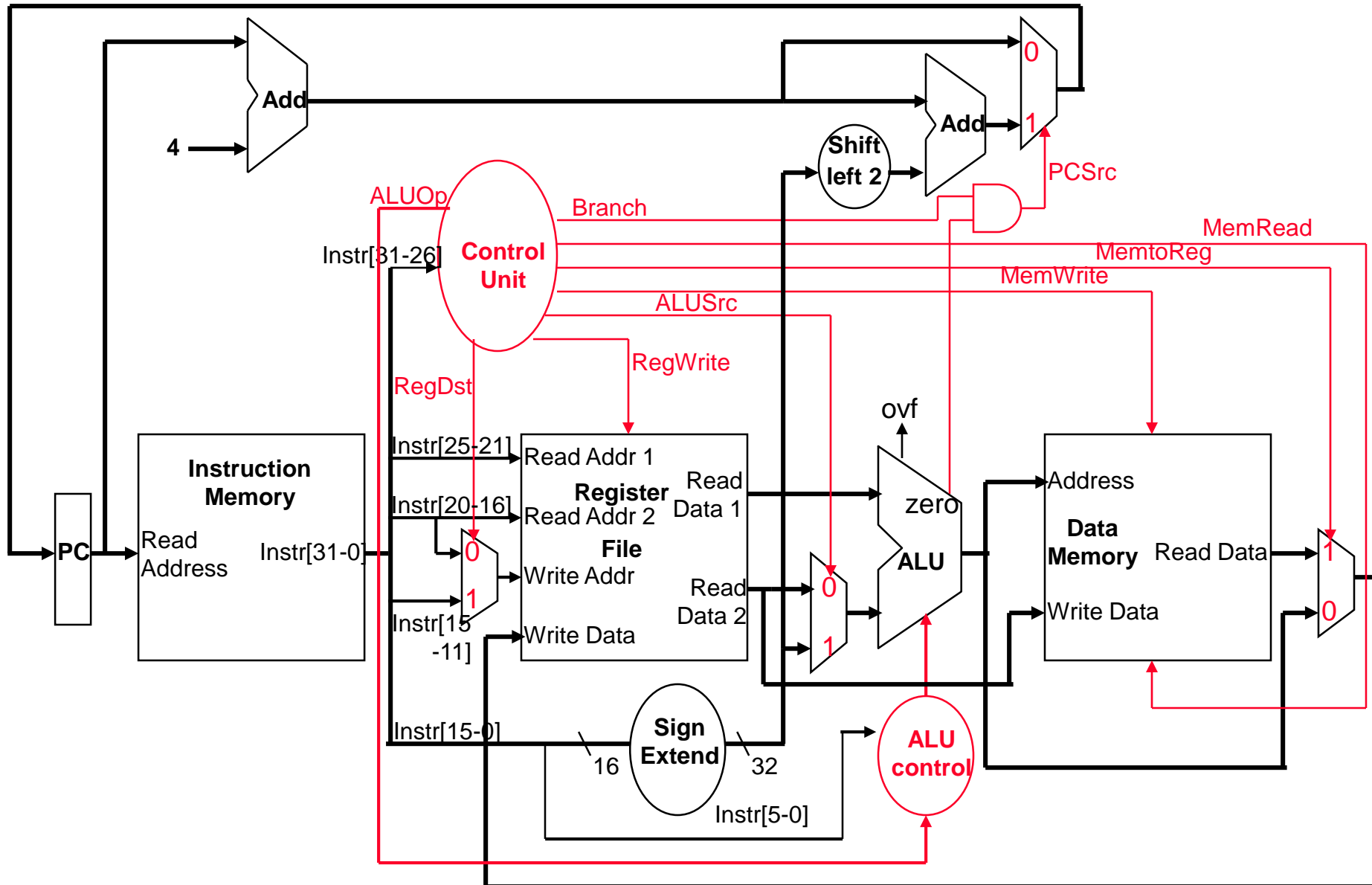
# Single Cycle Datapath with Control Unit




# R-type Instruction Data/Control Flow

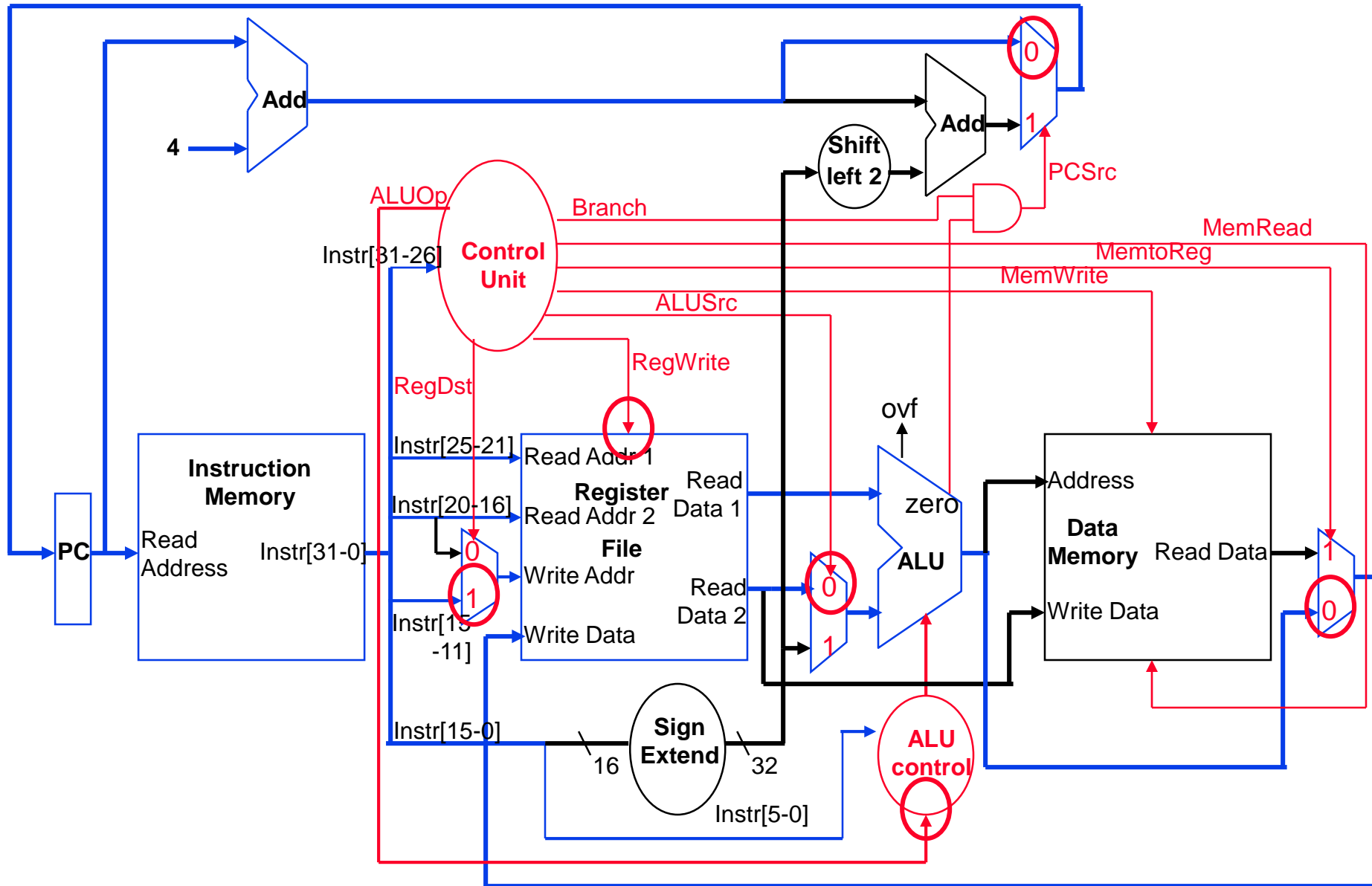
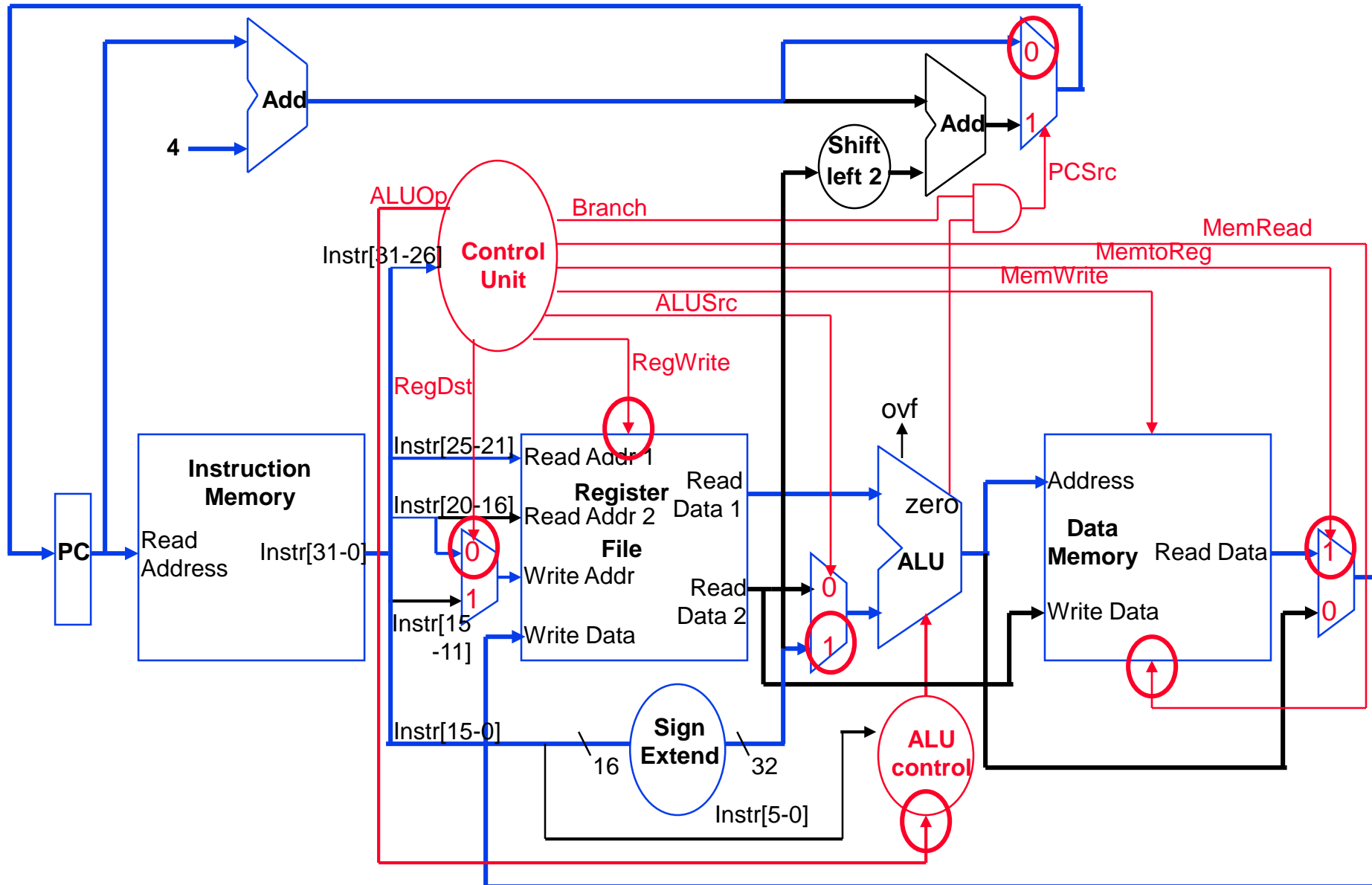
# Load Word Instruction Data/Control Flow



# Branch Instruction Data/Control Flow

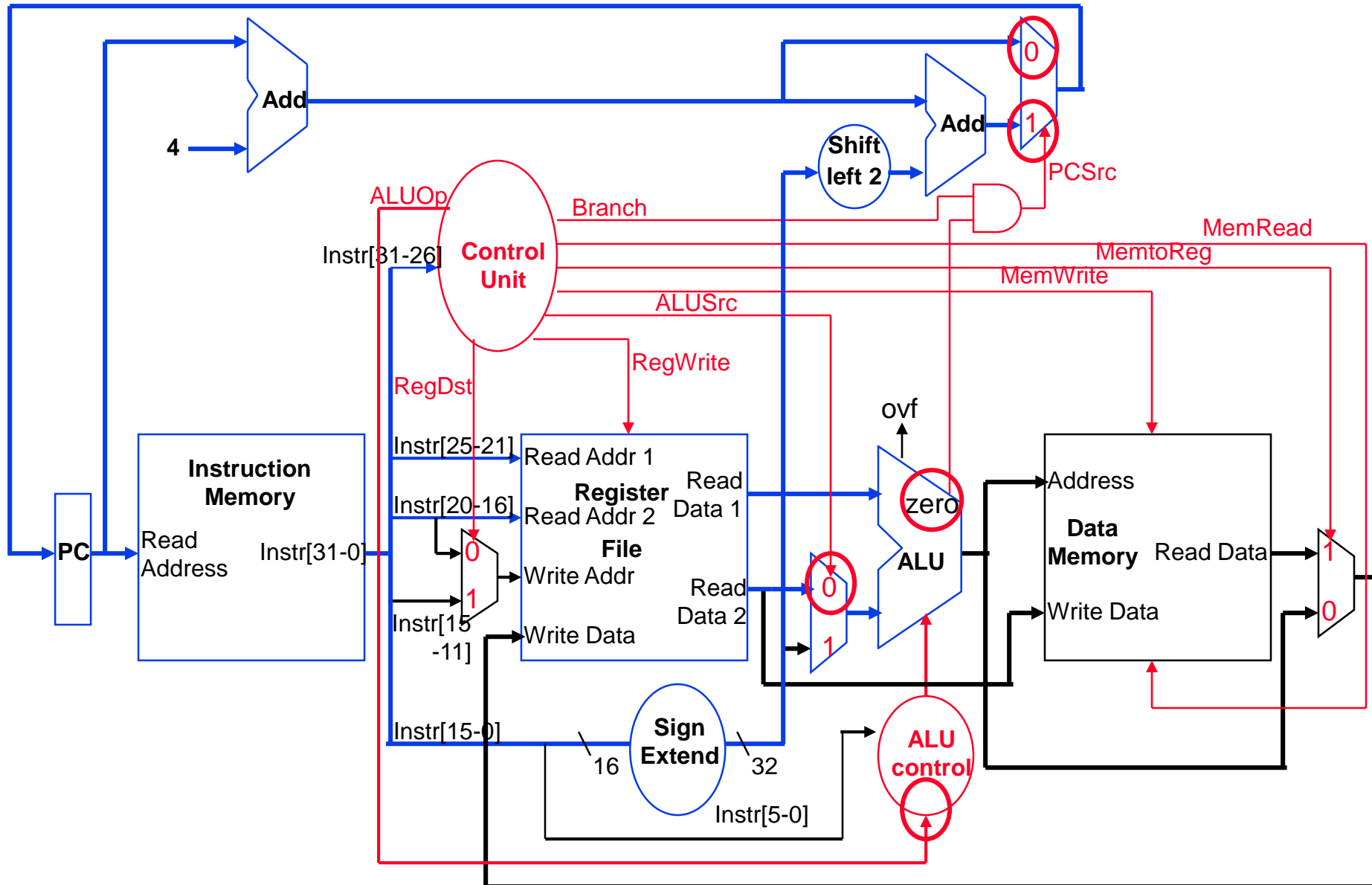



# Instruction Critical Paths


❑ What is the clock cycle time assuming negligible delays for muxes, control unit, sign extend, PC access, shift left 2, wires, setup and hold times except:

- Instruction and Data Memory (200 ps)
- ALU and adders (200 ps)
- Register File access (reads or writes) (100 ps)

Instr.	I Mem	Reg Rd	ALU Op	D Mem	Reg Wr	Total
R-type	200	100	200		100	600
load	200	100	200	200	100	800
store	200	100	200	200		700
beq	200	100	200			500
jump	200					200
 
# Single (Clock) Cycle Implementation

- ❑ Uses the clock cycle inefficiently – the clock cycle must be timed to accommodate the **slowest** instruction
  - especially problematic for more complex instructions like floating point multiply



- ❑ May be wasteful of area since some functional units (e.g., adders) must be duplicated since they can not be shared during a clock cycle

but

- ❑ Is simple and easy to understand

# Summary

---