
Chap. 4 The Processor


Part A – Simple Implementation

Introduction	244	
Logic Design Conventions	248	
Building a Datapath	251	
A Simple Implementation Scheme	259	
An Overview of Pipelining	272	
Pipelined Datapath and Control	286	
Data Hazards: Forwarding versus Stalling	303	
Control Hazards	316	
Exceptions	325	
Parallelism via Instructions	332	
Real Stuff: The ARM Cortex-A8 and Intel Core i7 Pipelines	344	
Going Faster: Instruction-Level Parallelism and Matrix Multiply	351	
Advanced Topic: An Introduction to Digital Design Using a Hardware Design Language to Describe and Model a Pipeline and More Pipelining Illustrations	354	
Fallacies and Pitfalls	355	
Concluding Remarks	356	
Historical Perspective and Further Reading	357	
Exercises	357	

** NUS, Aaron Tan 교수의 강의자료를 일부 포함하고 있습니다. **



Instruction Execution Cycle (Basic)

 

Fetch:

- Get instruction from memory
- Address is in **P**rogram **C**ounter (PC) Register

Decode:

- Find out the operation required

Operand Fetch:

- Get operand(s) needed for operation

Execute:

- Perform the required operation

Result Write (Store):

- Store the result of the operation



The Processor


❑ 2 Major Components for a processor

● Datapath

- Performs the arithmetic, logical and memory operations
- Collection of components that process data
Arithmetic Logic Unit(ALU), Shifters, Registers, multipliers

● Control

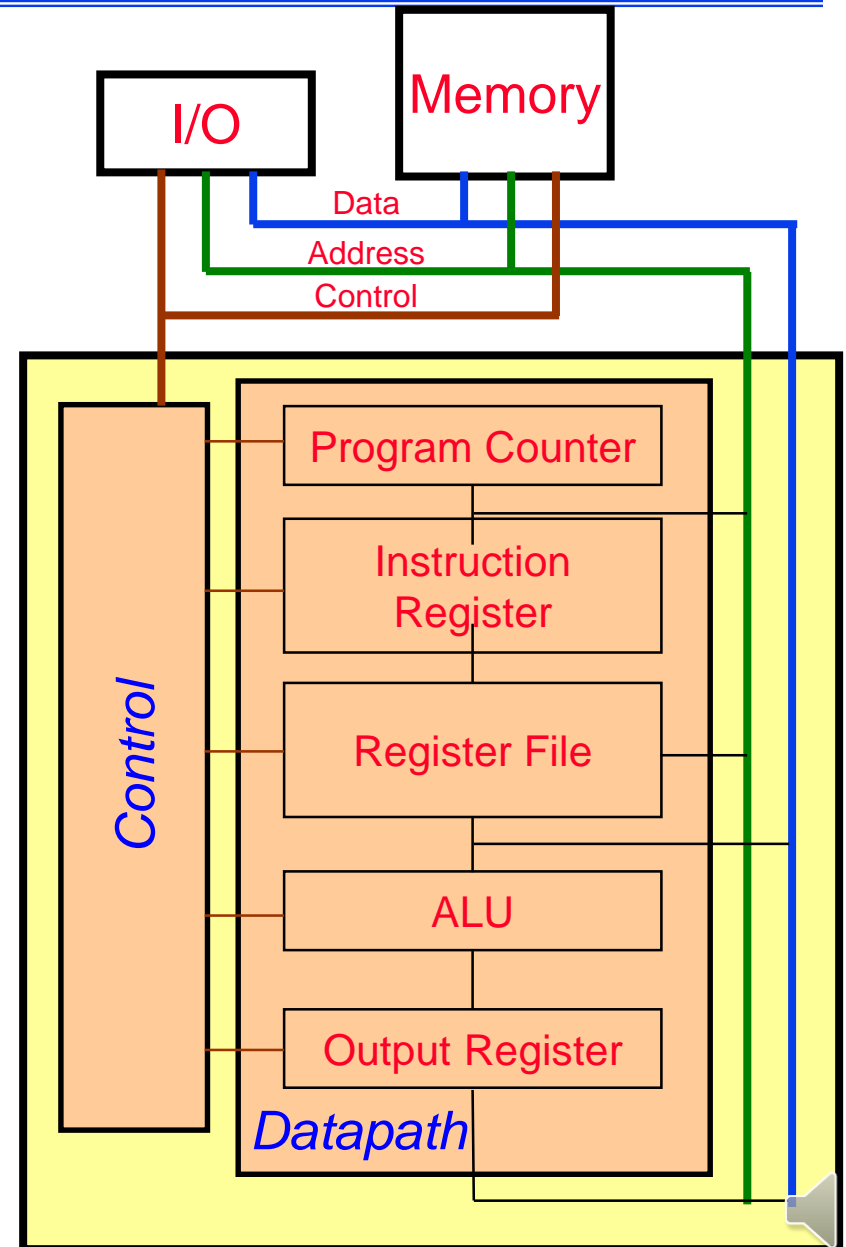- Tells the datapath, memory and I/O devices what to do according to program instructions




The Processor (Datapath & Control) Implementation

- ❑ Our implementation of the MIPS is simplified
 - arithmetic and logical instructions: **add, sub, and, or, slt**
 - memory-reference instructions: **lw, sw**
 - control flow instructions: **beq, bne, j**

- ❑ Generic implementation

 - use the PC to supply the instruction address and fetch the instruction from memory (and update the PC)
- decode the instruction (and read registers)
- execute the instruction



- ❑ All instructions (except **j**) use the ALU after reading the registers
 - *Arithmetic result : add, addi, sub, and, or*
 - *Memory address for load/store*
 - *Comparison result for branches*



Clocking Methodologies

- ❑ The **clocking methodology** defines when data in a state element is valid and stable relative to the clock
 - State elements - a memory element such as a register
 - Edge triggered - all state changes occur on a clock edge

- ❑ Typical execution
 - read contents of state elements
 - send values through combinational logic
 - write results to one or more state elements




Register Transfer Language and Clocking

Register transfer in RTL:

$$R2 \leftarrow f(R1)$$

What Really Happens Physically

 

Two possible clocking methodologies : positively triggered or negatively triggered. This class uses the negatively-triggered.

Building a Datapath

- MIPS Instruction Execution
- Design changes:
 - Merge *Decode* and *Operand Fetch* – Decode is simple for MIPS
 - Split *Execute* into **ALU** (Calculation) and **Memory Access**

	<code>add \$3, \$1, \$2</code>	<code>lw \$3, 20(\$1)</code>	<code>beq \$1, \$2, label</code>
Fetch	Read inst. at [PC]	Read inst. at [PC]	Read inst. at [PC]
Decode & Operand Fetch	<ul style="list-style-type: none"> ○ Read [\$1] as <i>opr1</i> ○ Read [\$2] as <i>opr2</i> 	<ul style="list-style-type: none"> ○ Read [\$1] as <i>opr1</i> ○ Use 20 as <i>opr2</i> 	<ul style="list-style-type: none"> ○ Read [\$1] as <i>opr1</i> ○ Read [\$2] as <i>opr2</i>
ALU	$Result = opr1 + opr2$	$MemAddr = opr1 + opr2$	$Taken = (opr1 == opr2) ?$ $Target = (PC+4) + ofst \times 4$
Memory Access		Use <i>MemAddr</i> to read from memory	
Result Write	<i>Result</i> stored in \$3	<i>Memory data</i> stored in \$3	if (<i>Taken</i>) $PC = Target$


opr = operand **MemAddr** = Memory Address **ofst** = offset



Fetching Instructions

❑ Fetching instructions involves

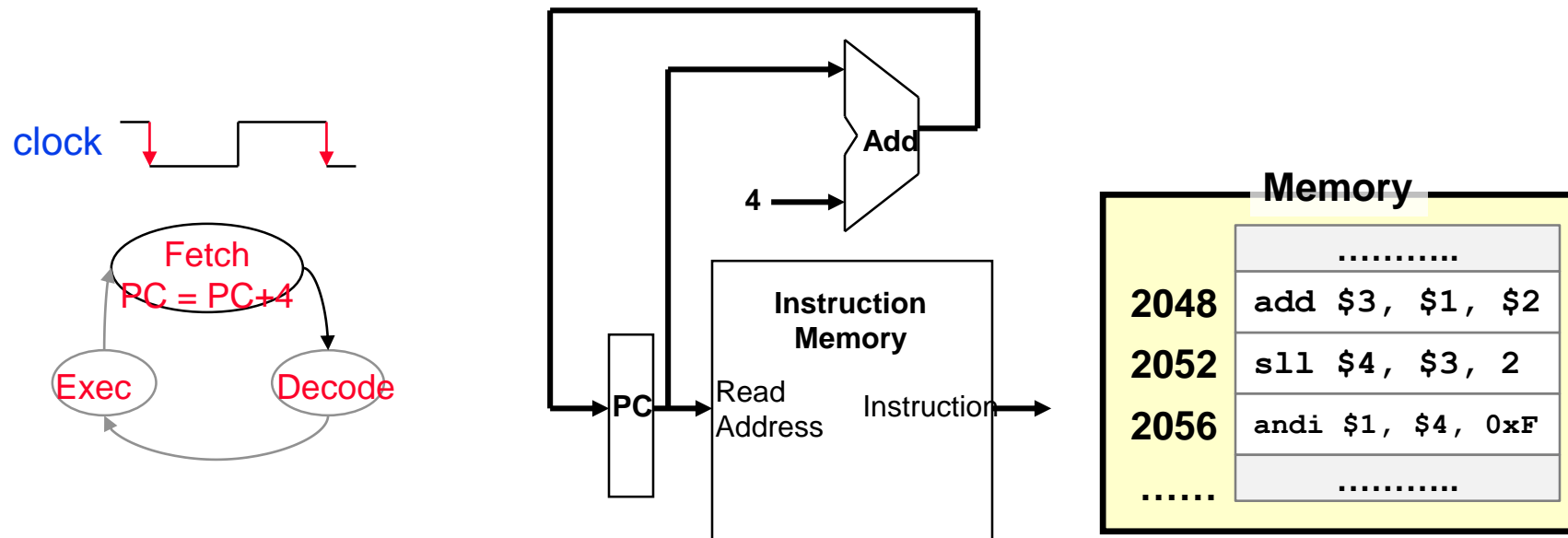- reading the instruction from the Instruction Memory
- updating the PC value to be the address of the next (sequential) instruction




- PC is updated every clock cycle, so it does not need an explicit write control signal just a clock signal
- Reading from the Instruction Memory is a combinational activity, so it doesn't need an explicit read control signal



Decoding Instructions

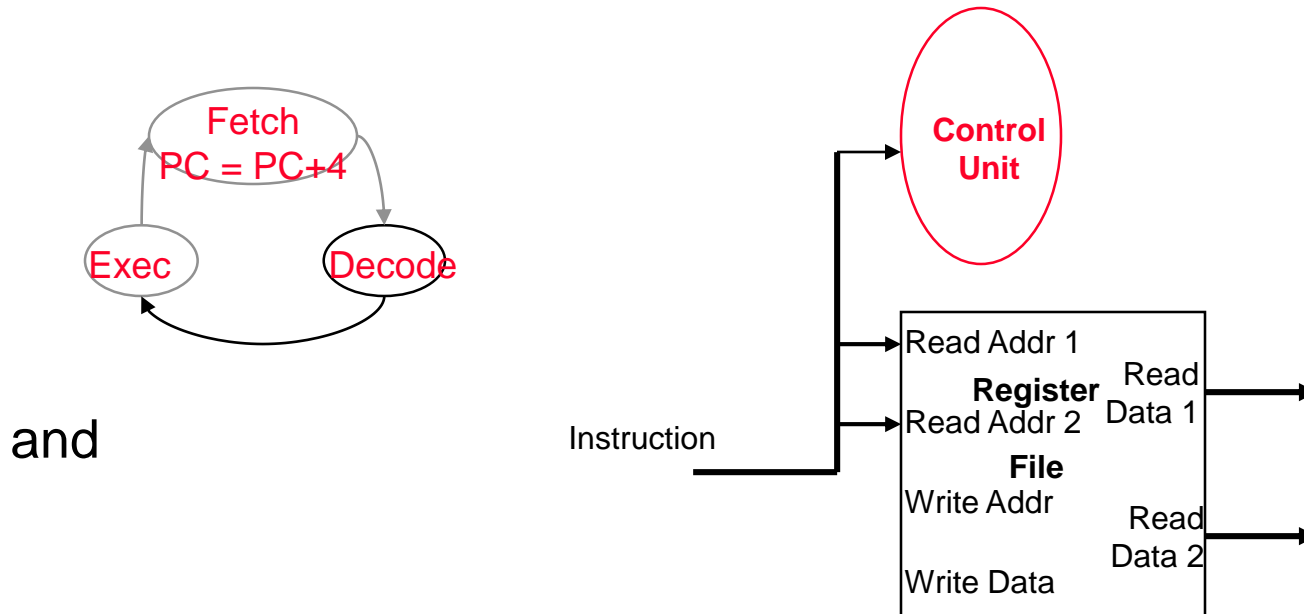
- ❑ Decoding instructions involves
 - sending the fetched instruction's opcode and function field bits to the control unit



- reading two values from the Register File
 - Register File addresses are contained in the instruction




Decode Stage: R-Format Instruction

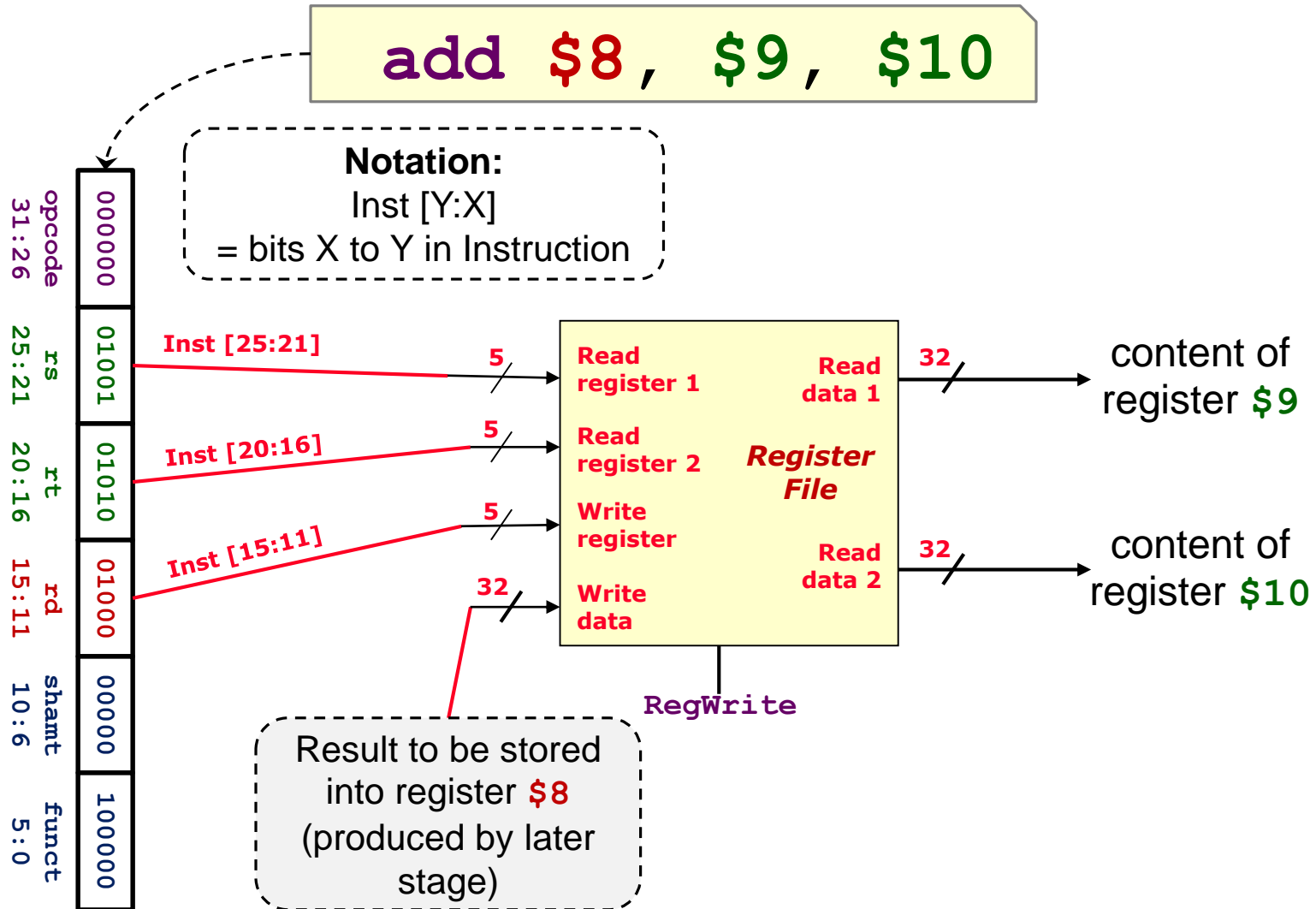


Decode Stage: Load Word Instruction

lw \$21, -50(\$22)

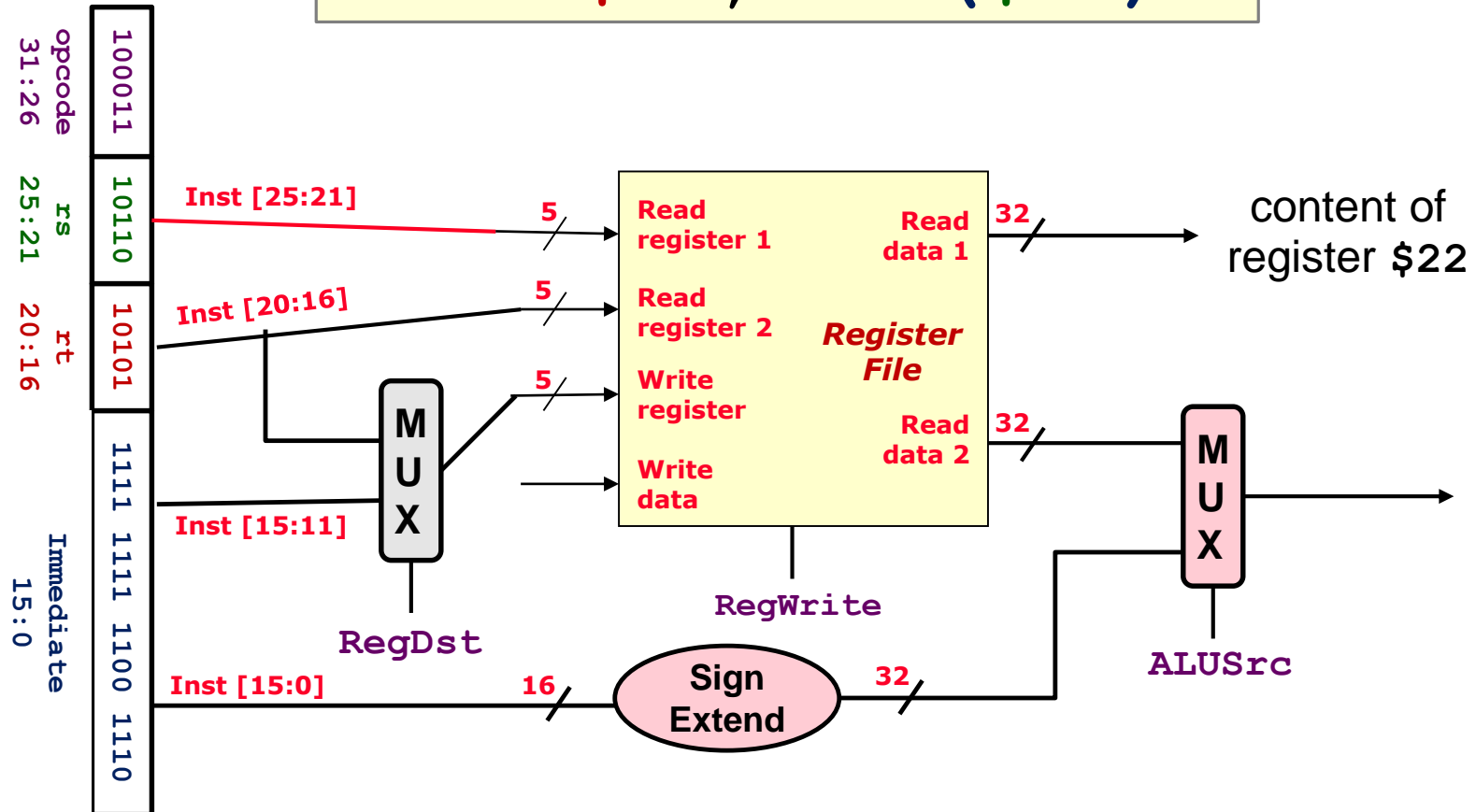


Decode Stage: Branch Instruction


 


Executing R Format Operations

 □ R format operations (**add**, **sub**, **slt**, **and**, **or**)



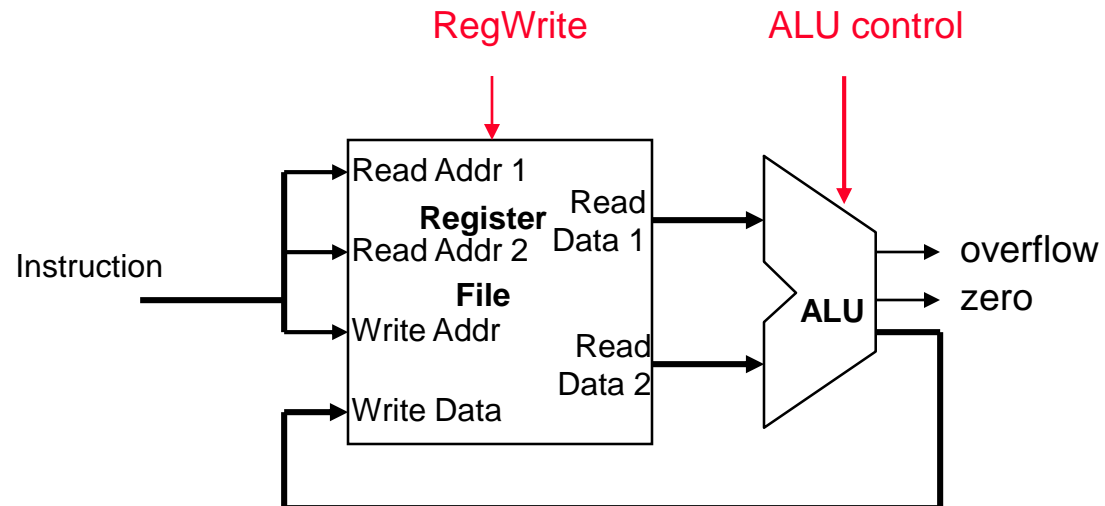 - perform operation (**op** and **funct**) on values in **rs** and **rt**
- store the result back into the Register File (into location **rd**)




- Note that Register File is not written every cycle (e.g. **sw**), so we need an explicit write control signal for the Register File

Executing Load and Store Operations

□ Load and store operations involves

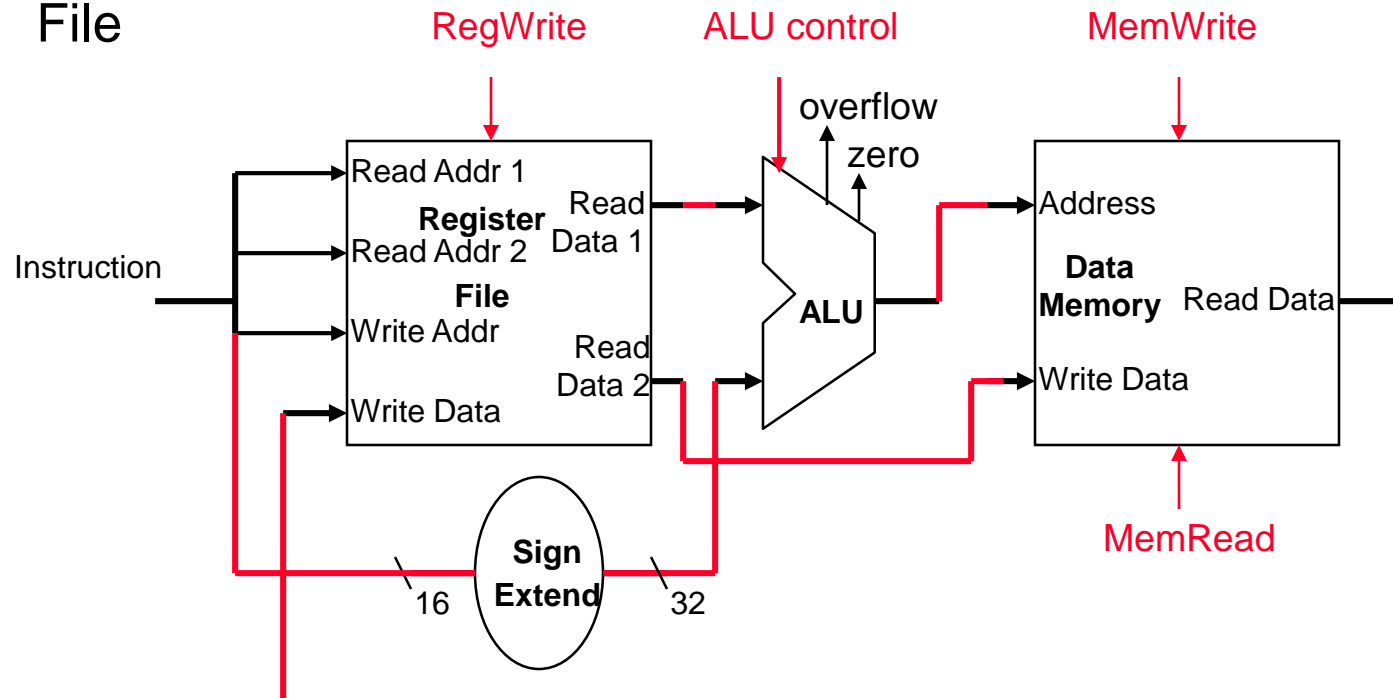
- **compute memory address** by adding the base register (read from the Register File during decode) to the 16-bit signed-extended offset field in the instruction
- **store** value (read from the Register File during decode) written to the Data Memory
- **load** value, read from the Data Memory, written to the Register File



Executing Branch Operations

❑ Branch operations involves

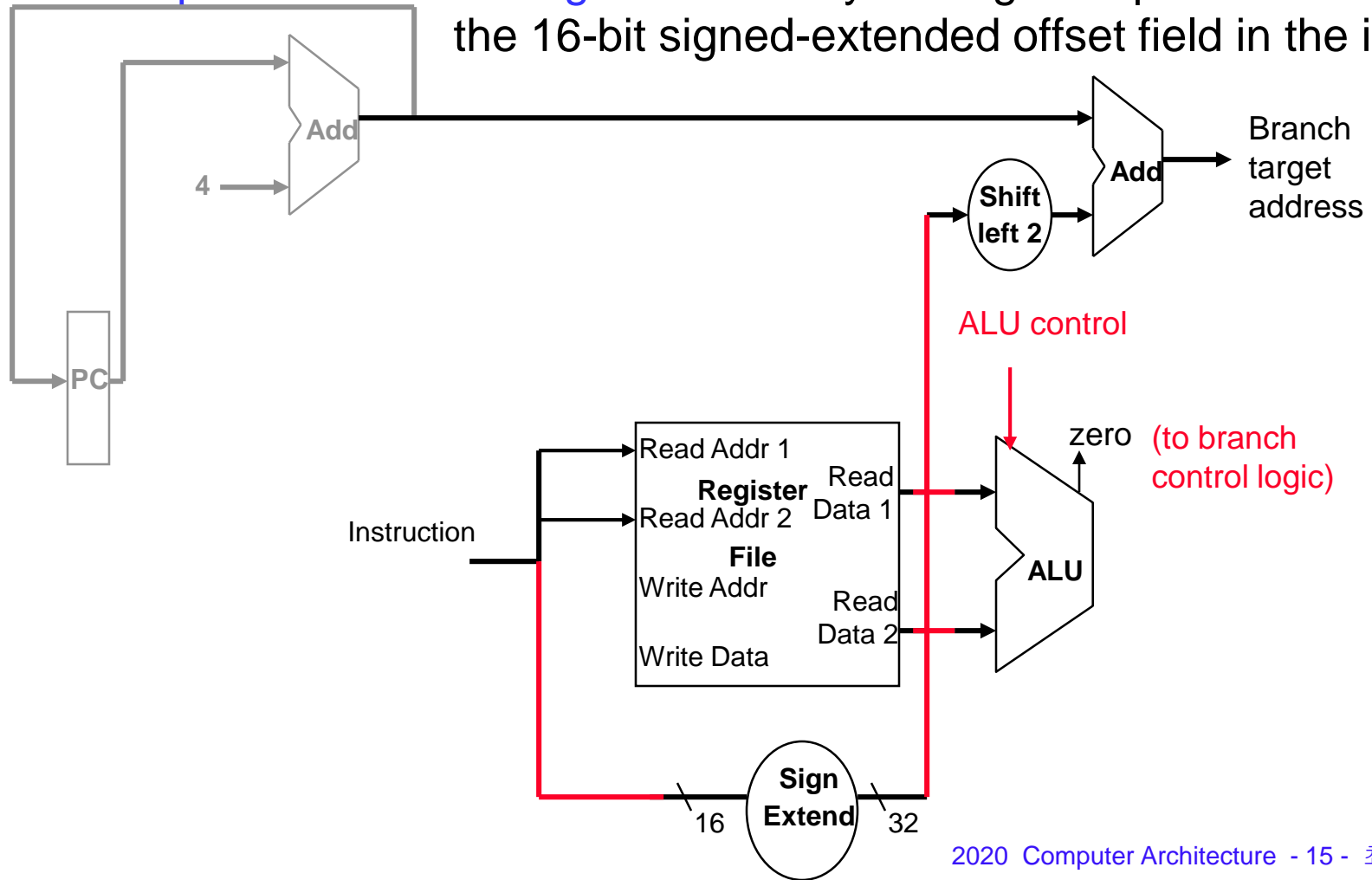- compare the operands read from the Register File during decode for equality (**zero** ALU output)
- compute the branch target address by adding the updated PC to the 16-bit signed-extended offset field in the instr



Creating a Single Datapath from the Parts

- ❑ Assemble the datapath segments and add control lines and multiplexors as needed
- ❑ **Single cycle** design – fetch, decode and execute each instructions in **one** clock cycle
 - no datapath resource can be used more than once per instruction, so some must be duplicated (e.g., separate Instruction Memory and Data Memory, several adders)
 - **multiplexors** needed at the input of shared elements with control lines to do the selection
 - write signals to control writing to the Register File and Data Memory
- ❑ Cycle time is determined by length of the longest path



Fetch, R, and Memory Access Portions

